



# **COL215 DIGITAL LOGIC AND SYSTEM DESIGN**

Signed Numbers,

Fast addition

06 September 2017

# Representing signed integers

## Sign Magnitude

000	= +0
001	= +1
010	= +2
011	= +3
100	= -0
101	= -1
110	= -2
111	= -3

Sign leftmost bit

Balance Yes

Zeros Not unique

## 1's Complement

000	= +0
001	= +1
010	= +2
011	= +3
100	= -3
101	= -2
110	= -1
111	= -0

leftmost bit

Yes

Not unique

## 2's Complement

000	= +0
001	= +1
010	= +2
011	= +3
100	= -4
101	= -3
110	= -2
111	= -1

leftmost bit

No

Unique

# 16 bit signed integers

$$0000\ 0000\ 0000\ 0000_2 = 0_{10}$$

$$0000\ 0000\ 0000\ 0001_2 = +1_{10}$$

$$0000\ 0000\ 0000\ 0010_2 = +2_{10}$$

.....

$$0111\ 1111\ 1111\ 1110_2 = + (2^{15}-2)_{10}$$

$$0111\ 1111\ 1111\ 1111_2 = + (2^{15}-1)_{10}$$

$$1000\ 0000\ 0000\ 0000_2 = - (2^{15})_{10}$$

$$1000\ 0000\ 0000\ 0001_2 = - (2^{15}-1)_{10}$$

$$1000\ 0000\ 0000\ 0010_2 = - (2^{15}-2)_{10}$$

.....

$$1111\ 1111\ 1111\ 1101_2 = -3_{10}$$

$$1111\ 1111\ 1111\ 1110_2 = -2_{10}$$

$$1111\ 1111\ 1111\ 1111_2 = -1_{10}$$

*maxint = 32,767*

*minint = -32,768*

# 32 bit signed integers

0000 0000 0000 0000 0000 0000 0000 0000<sub>2</sub> = 0<sub>10</sub>

0000 0000 0000 0000 0000 0000 0000 0001<sub>2</sub> = + 1<sub>10</sub>

0000 0000 0000 0000 0000 0000 0000 0010<sub>2</sub> = + 2<sub>10</sub>

.....

0111 1111 1111 1111 1111 1111 1111 1110<sub>2</sub> = + (2<sup>31</sup>-2)<sub>10</sub> *maxint = 2,147,483,647*

0111 1111 1111 1111 1111 1111 1111 1111<sub>2</sub> = + (2<sup>31</sup>-1)<sub>10</sub>

1000 0000 0000 0000 0000 0000 0000 0000<sub>2</sub> = - (2<sup>31</sup>)<sub>10</sub>

1000 0000 0000 0000 0000 0000 0000 0001<sub>2</sub> = - (2<sup>31</sup>-1)<sub>10</sub>

1000 0000 0000 0000 0000 0000 0000 0010<sub>2</sub> = - (2<sup>31</sup>-2)<sub>10</sub>

..... *minint = -2,147,483,648*

1111 1111 1111 1111 1111 1111 1111 1101<sub>2</sub> = - 3<sub>10</sub>

1111 1111 1111 1111 1111 1111 1111 1110<sub>2</sub> = - 2<sub>10</sub>

1111 1111 1111 1111 1111 1111 1111 1111<sub>2</sub> = - 1<sub>10</sub>

# Add/Subtract signed integers

- 2's complement representation makes it easy - add/subtract ignoring sign!

0111 [ 7]	0101 [ 5]	0010 [ 2]
+ 1110 [-2]	- 1110 [-2]	- 0101 [ 5]
<hr/>		
0101 [ 5]	0111 [ 7]	1101 [-3]

Why?

Representation of  $-X$  is nothing but  $2^n - X$

# Two's complement representation

- Represent “- 3”

$$\begin{array}{rcl} 10000 [2^4] & \text{alternatively} & 1100 [\text{invert } 3] \\ - 0011 [3] & & + 0001 [1] \\ \hline 1101 [-3] & & 1101 [-3] \end{array}$$

- Negating a two's complement number (+ve or -ve): invert all bits and add 1
- Subtraction using addition:  $X - Y = X + Y' + 1$



# Converting n bit numbers into numbers with more than n bits

Required when operands are of mixed size


For example, adding a signed half word to a signed full word

- copy the most significant bit (the sign bit) into the other bits

0010  $\Rightarrow$  0000 0010


1010  $\Rightarrow$  1111 1010

# Overflow in unsigned $s = a + b$

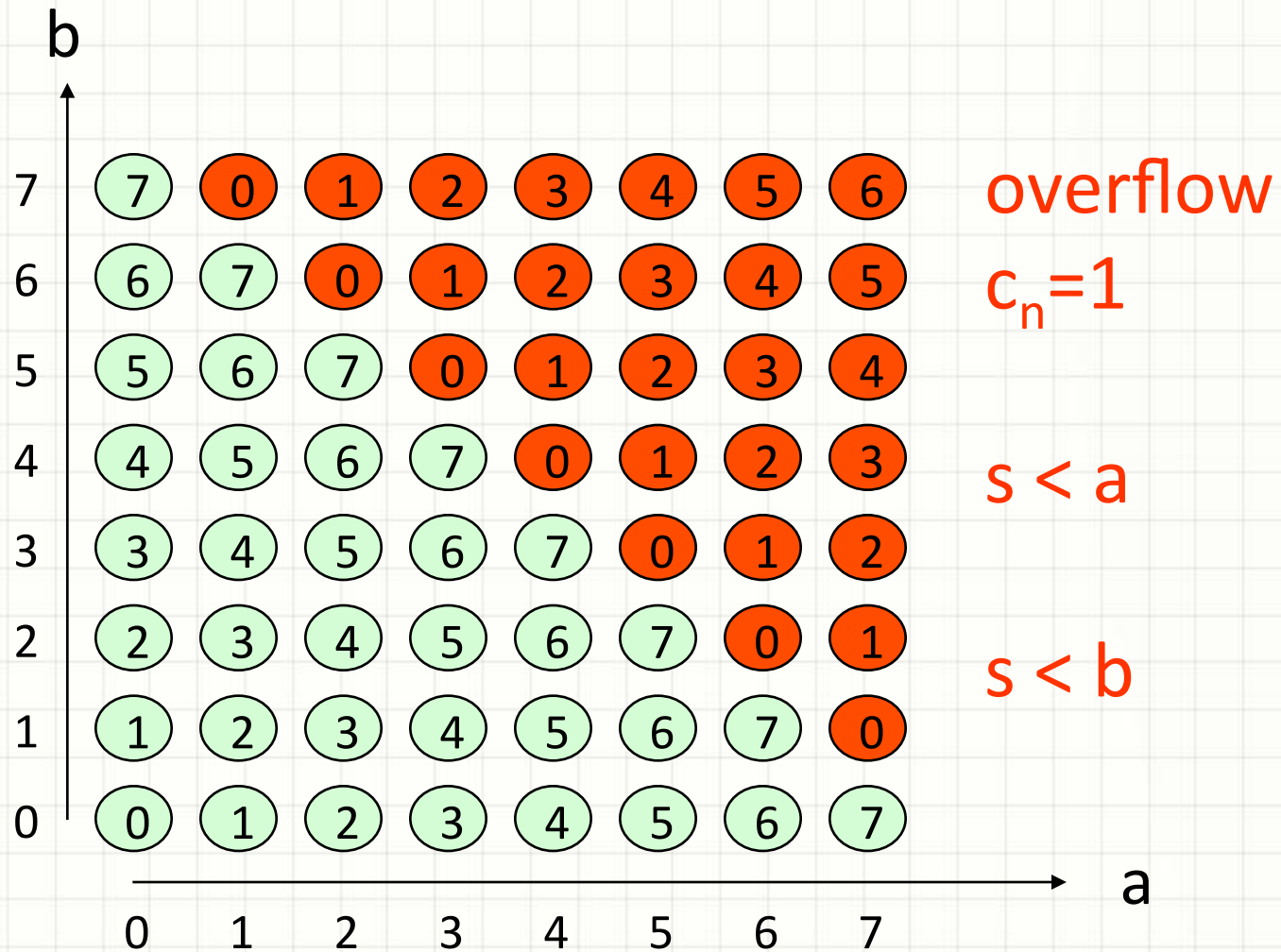




# Overflow in unsigned $s = a + b' + 1$

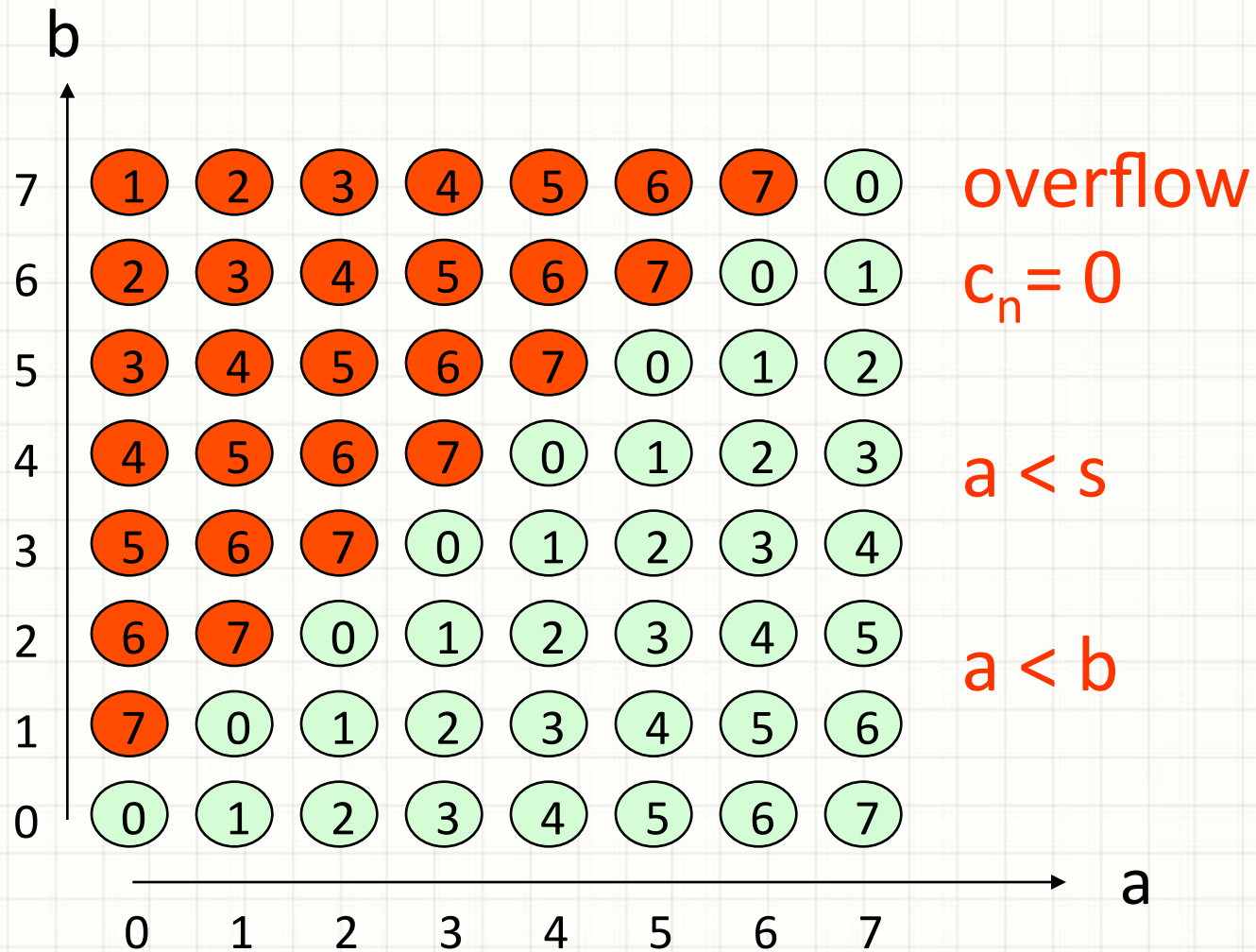

# Overflow in signed $s = a + b$

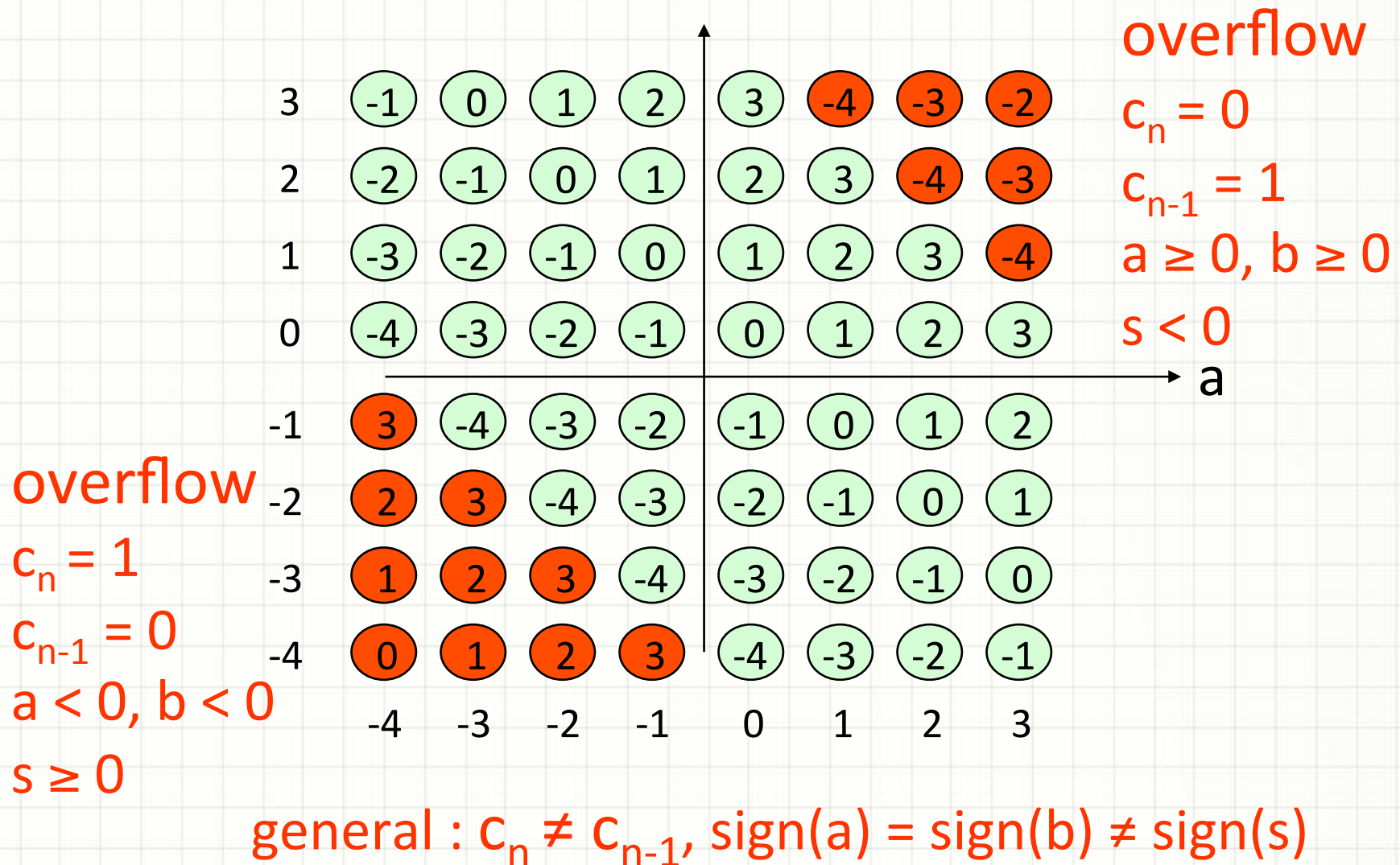

# Overflow in signed $s = a + b' + 1$


overflow

$$c_n = 1$$

$$c_{n-1} = 0$$

$$a < 0, b \geq 0$$

$$s \geq 0$$

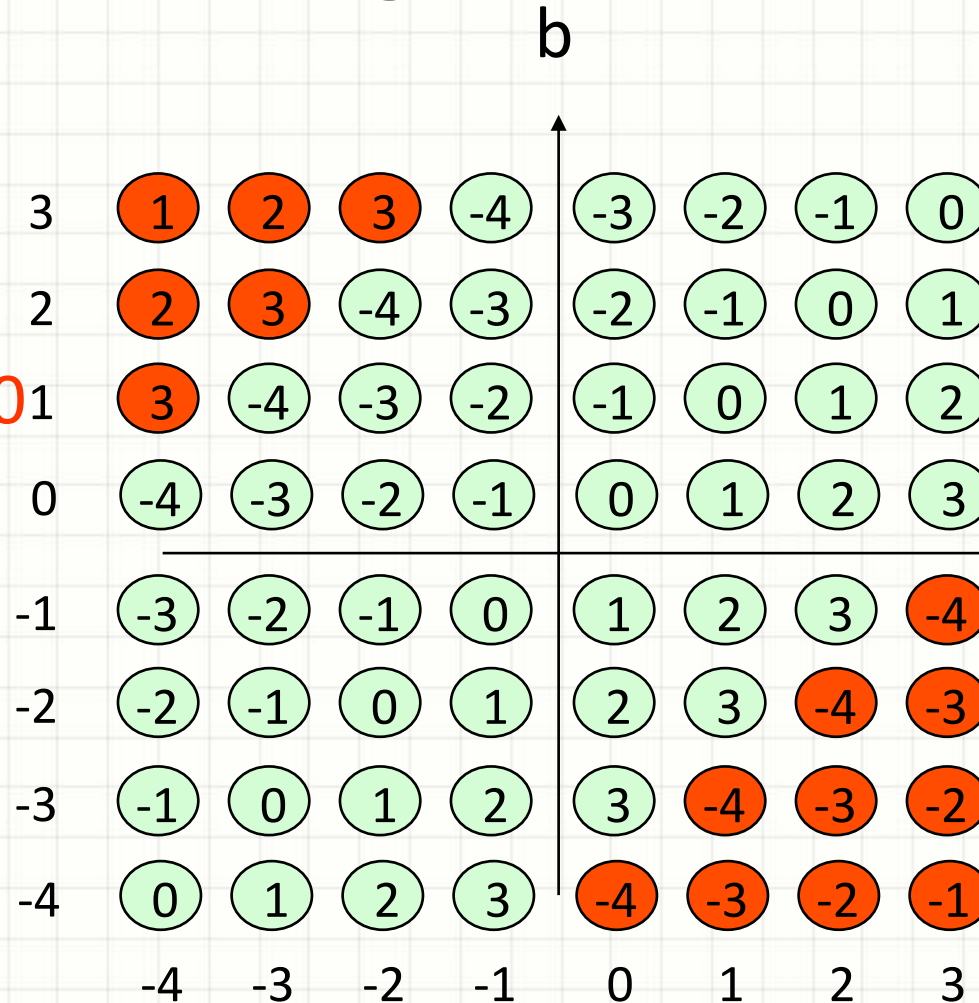

overflow

$$c_n = 0$$

$$c_{n-1} = 1$$



$$a \geq 0, b < 0$$

$$s < 0$$

general :  $c_n \neq c_{n-1}, \text{sign}(a) \neq \text{sign}(b) = \text{sign}(s)$

# Adder circuit

n bit adder =  
array of n full adders

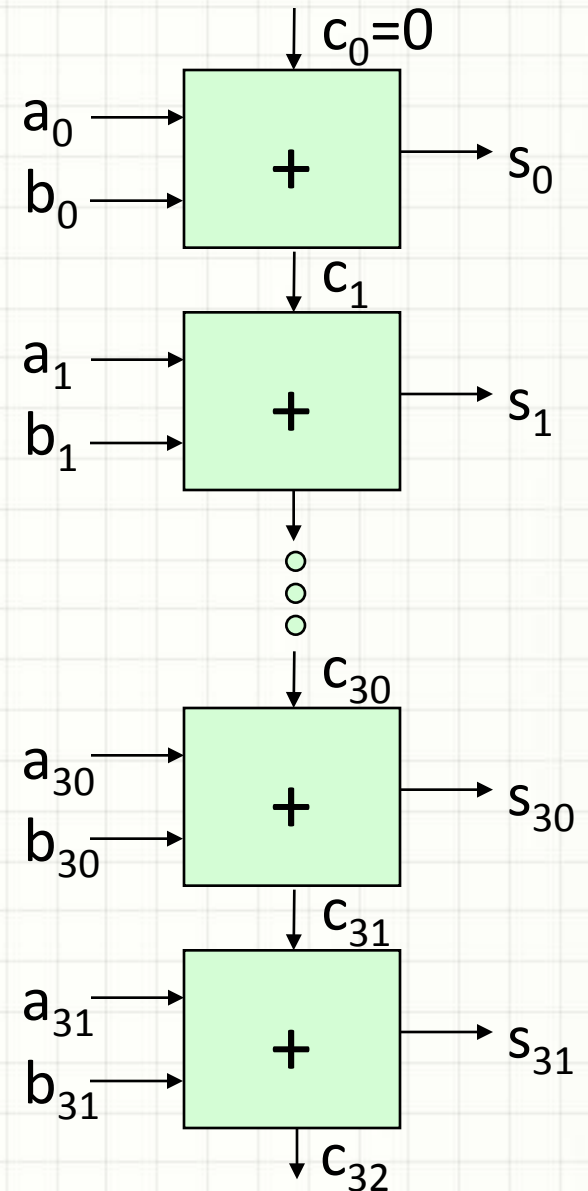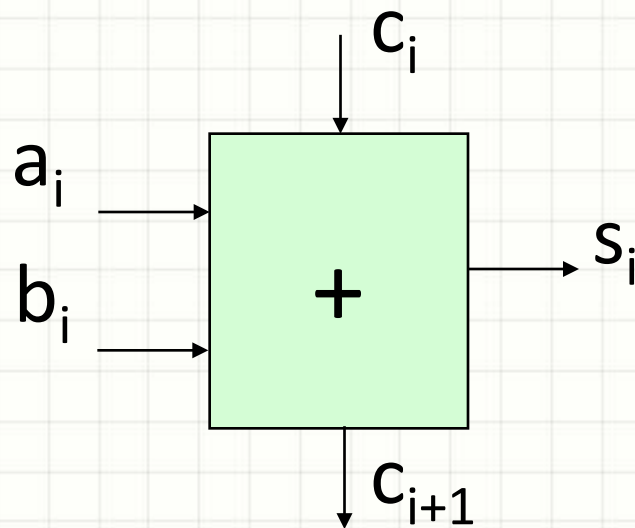

# One bit adder implementation



$a_i$	$b_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$
  
# Combining addition and subtraction

Use a multiplexer circuit and initial carry





# Boolean expressions for adder

$$\begin{aligned}s_i &= a_i' b_i' c_i + a_i' b_i c_i' + a_i b_i' c_i' + a_i b_i c_i \\ &= a_i \oplus b_i \oplus c_i\end{aligned}$$

alternatively,

$$\begin{aligned}s_i &= (a_i' b_i' + a_i b_i) c_i + (a_i b_i' + a_i' b_i) c_i' \\ &= t_i' c_i + t_i c_i' \quad \text{where } t_i = a_i b_i' + a_i' b_i \\ &= (a_i \oplus b_i) \oplus c_i\end{aligned}$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i = a_i b_i + (a_i + b_i) c_i$$

# Performance considerations

- Delay along a path depends on
  - the number of gates in the path
- Delay of an individual gate depends on
  - the number of inputs to the gate
- Path(s) with maximum delay is(are) called “critical path(s)”
- Current design: simple and slow
  - clever changes can improve performance

# Speed of ripple carry adder (carry propagate adder)

- Ripple is caused because  $c_{i+1}$  is generated from  $c_i$

$$c_{i+1} = b_i c_i + a_i c_i + a_i b_i$$

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$c_2 = b_1 c_1 + a_1 c_1 + a_1 b_1$$

$$c_3 = b_2 c_2 + a_2 c_2 + a_2 b_2$$

$$c_4 = b_3 c_3 + a_3 c_3 + a_3 b_3$$

- Can  $c_{i+1}$  be generated directly from  $a_0..a_i$ ,  $b_0..b_i$ , and  $c_0$ ?

$c_{i+1}$  in terms of  $a_0.. a_i$ ,  $b_0.. b_i$ , and  $c_0$

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$c_2 = b_1 c_1 + a_1 c_1 + a_1 b_1 =$$

$$b_0 b_1 c_0 + a_0 b_1 c_0 + a_0 b_0 b_1 + a_1 b_0 c_0 + a_0 a_1 c_0 + a_0 a_1 b_0 + a_1 b_1$$

$$c_3 = b_2 c_2 + a_2 c_2 + a_2 b_2 =$$

$$b_0 b_1 b_2 c_0 + a_0 b_1 b_2 c_0 + a_0 b_0 b_1 b_2 + a_1 b_0 b_2 c_0 + a_0 a_1 b_2 c_0 + a_0 a_1 b_0 b_2 + a_1 b_1 b_2 + a_2 b_0 b_1 c_0 + a_0 a_2 b_1 c_0 + a_0 a_2 b_0 b_1 + a_1 a_2 b_0 c_0 + a_0 a_1 a_2 c_0 + a_0 a_1 a_2 b_0 + a_1 a_2 b_1 + a_2 b_2$$

$$c_4 = b_3 c_3 + a_3 c_3 + a_3 b_3 = \dots\dots$$

$c_{32}$  will have 4 billion terms !!

Effect of large fanin and fanout ??

# Carry-lookahead adder

- An approach in-between our two extremes
- Idea:
  - If we didn't know the value of carry-in, what could we do?
  - When would we always generate a carry?
$$g_i = a_i b_i$$
  - When would we propagate the carry?
$$p_i = a_i + b_i$$

# Carry-lookahead adder

Express carries using p's and g's

$$c_1 = p_0 c_0 + g_0$$

$$c_2 = p_1 c_1 + g_1 = p_1 p_0 c_0 + p_1 g_0 + g_1$$

$$c_3 = p_2 c_2 + g_2 = p_2 p_1 p_0 c_0 + p_2 p_1 g_0 + p_2 g_1 + g_2$$


$$c_4 = p_3 c_3 + g_3 =$$

$$p_3 p_2 p_1 p_0 c_0 + p_3 p_2 p_1 g_0 + p_3 p_2 g_1 + p_3 g_2 + g_3$$



Feasible! To what extent?



# 4 bit CLA adder

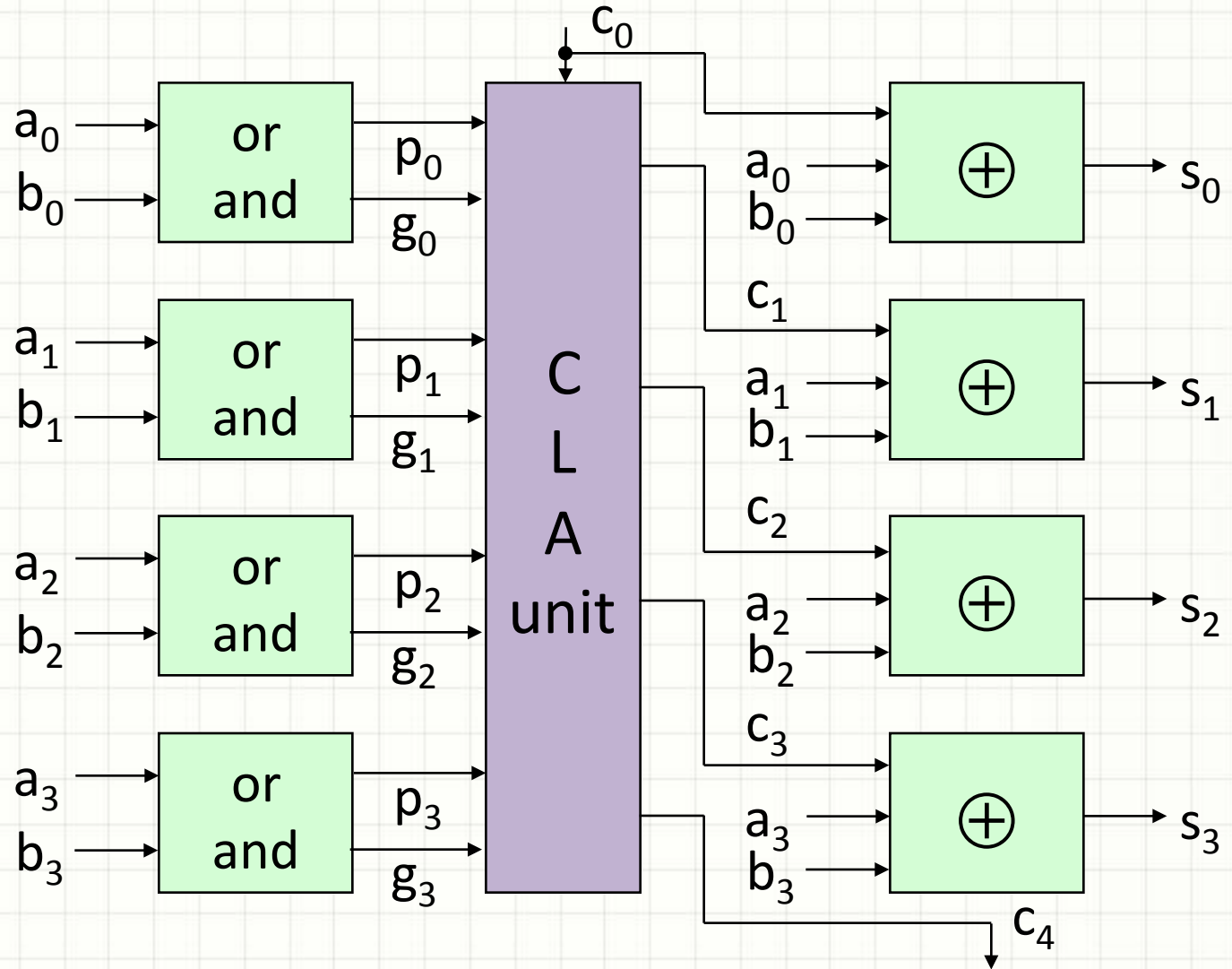


# 4 bit CLA adder abstraction

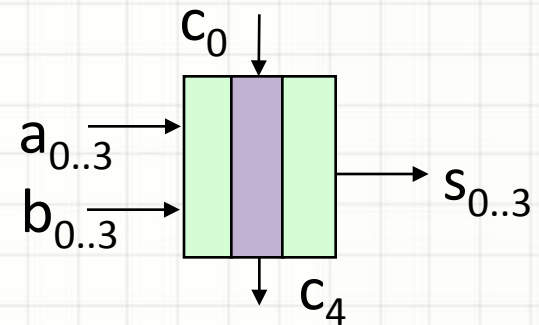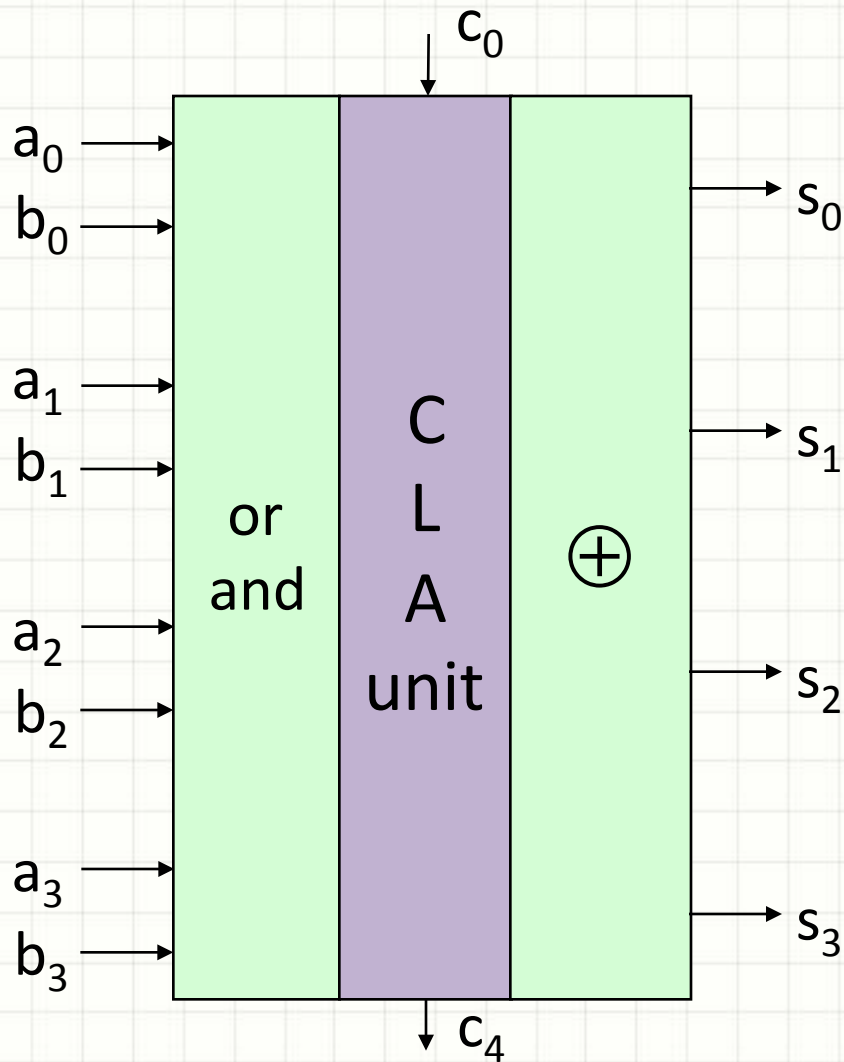

abstraction


# 16 bit addition with 4 bit CLAs

partial rippling of carry

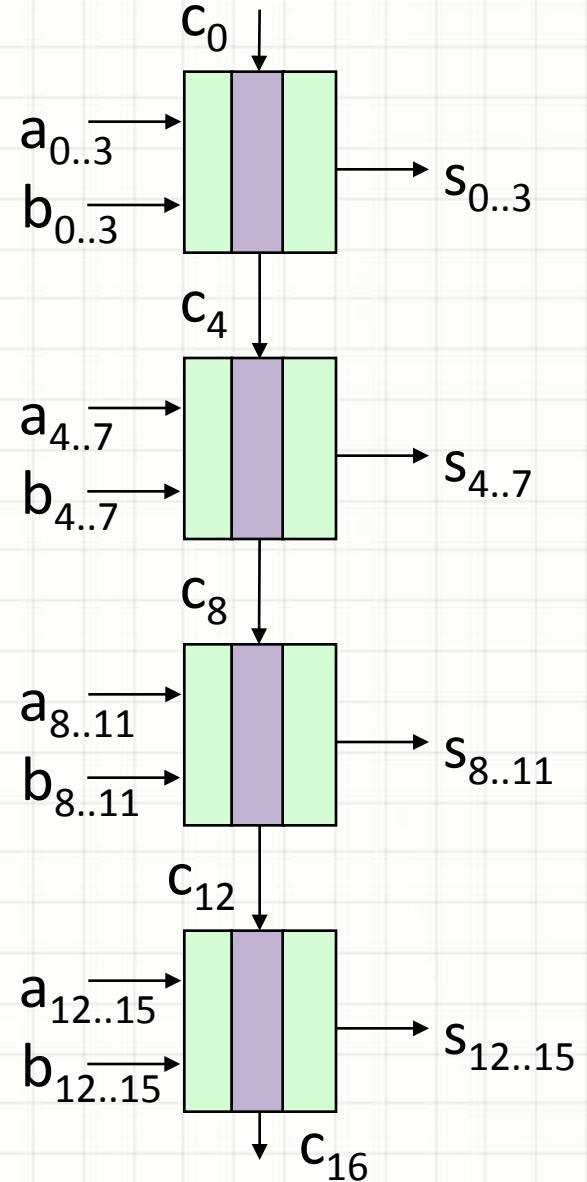

# 2 levels of look ahead

no rippling of carry

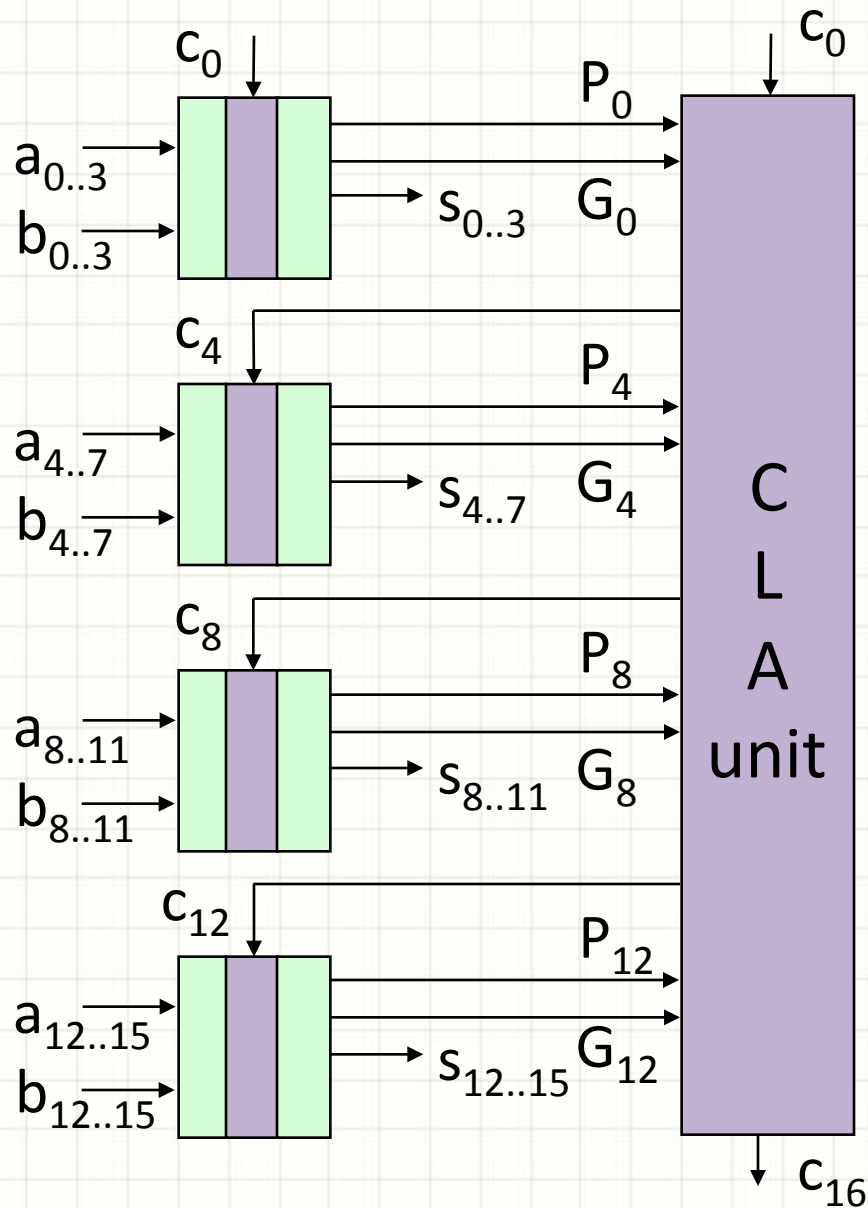

# Group propagate & generate

$$c_1 = p_0 c_0 + g_0$$

$$c_2 = p_1 c_1 + g_1 = p_1 p_0 c_0 + p_1 g_0 + g_1$$

$$c_3 = p_2 c_2 + g_2 = p_2 p_1 p_0 c_0 + p_2 p_1 g_0 + p_2 g_1 + g_2$$

$$c_4 = p_3 c_3 + g_3 =$$

$$p_3 p_2 p_1 p_0 c_0 + p_3 p_2 p_1 g_0 + p_3 p_2 g_1 + p_3 g_2 + g_3$$

$$P_0 = p_3 p_2 p_1 p_0$$

$$G_0 = p_3 p_2 p_1 g_0 + p_3 p_2 g_1 + p_3 g_2 + g_3$$

$$c_4 = P_0 c_0 + G_0$$

# Group propagate & generate

$$P_i = p_{i+3} p_{i+2} p_{i+1} p_i$$

$$G_i = p_{i+3} p_{i+2} p_{i+1} g_i + p_{i+3} p_{i+2} g_{i+1} + p_{i+3} g_{i+2} + g_{i+3}$$

$$c_4 = P_0 c_0 + G_0$$

$$c_8 = P_4 P_0 c_0 + P_4 G_0 + G_4$$

$$c_{12} = P_8 P_4 P_0 c_0 + P_8 P_4 G_0 + P_8 G_4 + G_8$$

$$c_{16} = P_{12} P_8 P_4 P_0 c_0 + P_{12} P_8 P_4 G_0 + P_{12} P_8 G_4 + P_{12} G_8 + G_{12}$$





**THANKS**