



# **COL215 DIGITAL LOGIC AND SYSTEM DESIGN**

Sequential Circuits



04 August 2017





# Lecture Outline


- Basic memory elements
- Gated latches
- Master-Slave flip-flops
- Edge triggered flip-flops

# Storage element design

  

# Gated SR Latch

  

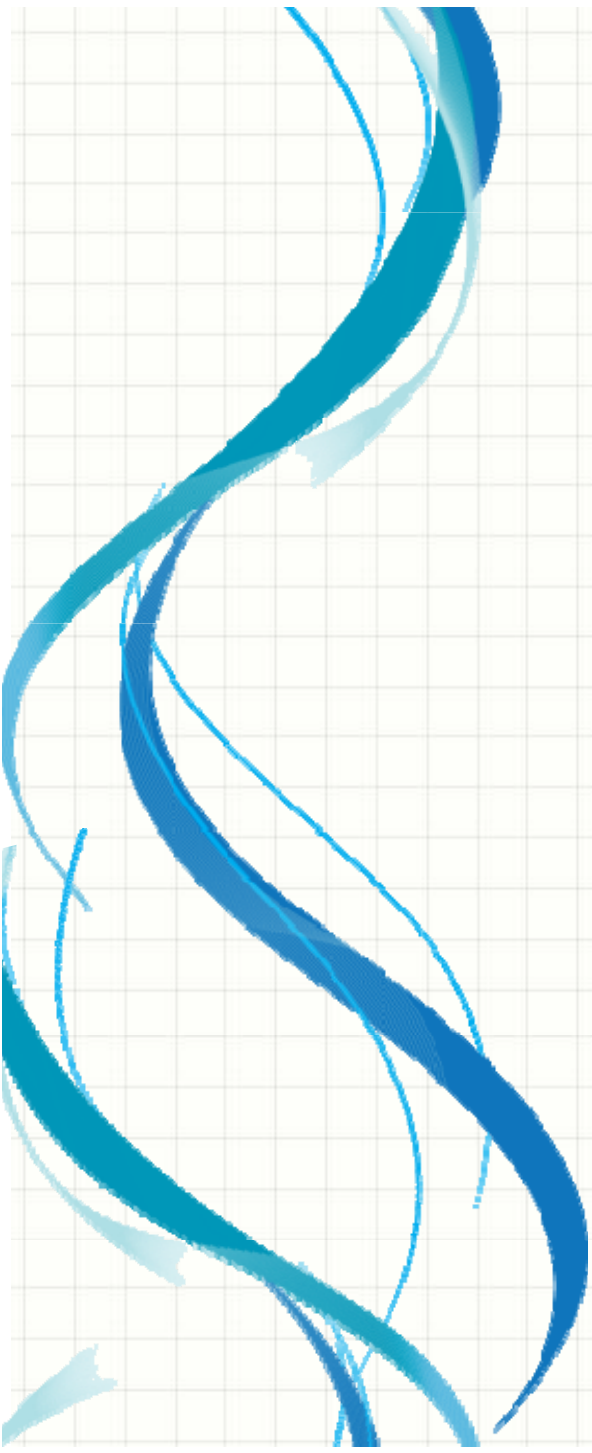

# Problems with SR latch design


- Problem of transition from  $(S = R = 1)$  to  $(S = R = 0)$   
uncertain output |  
oscillations | meta-stability
- Problem of change in S, R while  $C = 1$   
output change not timed with  
clock




# Solutions

- Don't connect S, R directly
  - $S = D, R = \overline{D}$
  - Gate R input with  $\overline{S}$  or vice versa
- Edge triggering, not level triggering
  - Master-slave flip-flop (8 gates)
  - Edge triggered flip-flop (6 gates)


# D Latch

 




# S overrides R

 



 


# Abstraction

  
 





# Master-Slave D Flip-Flop

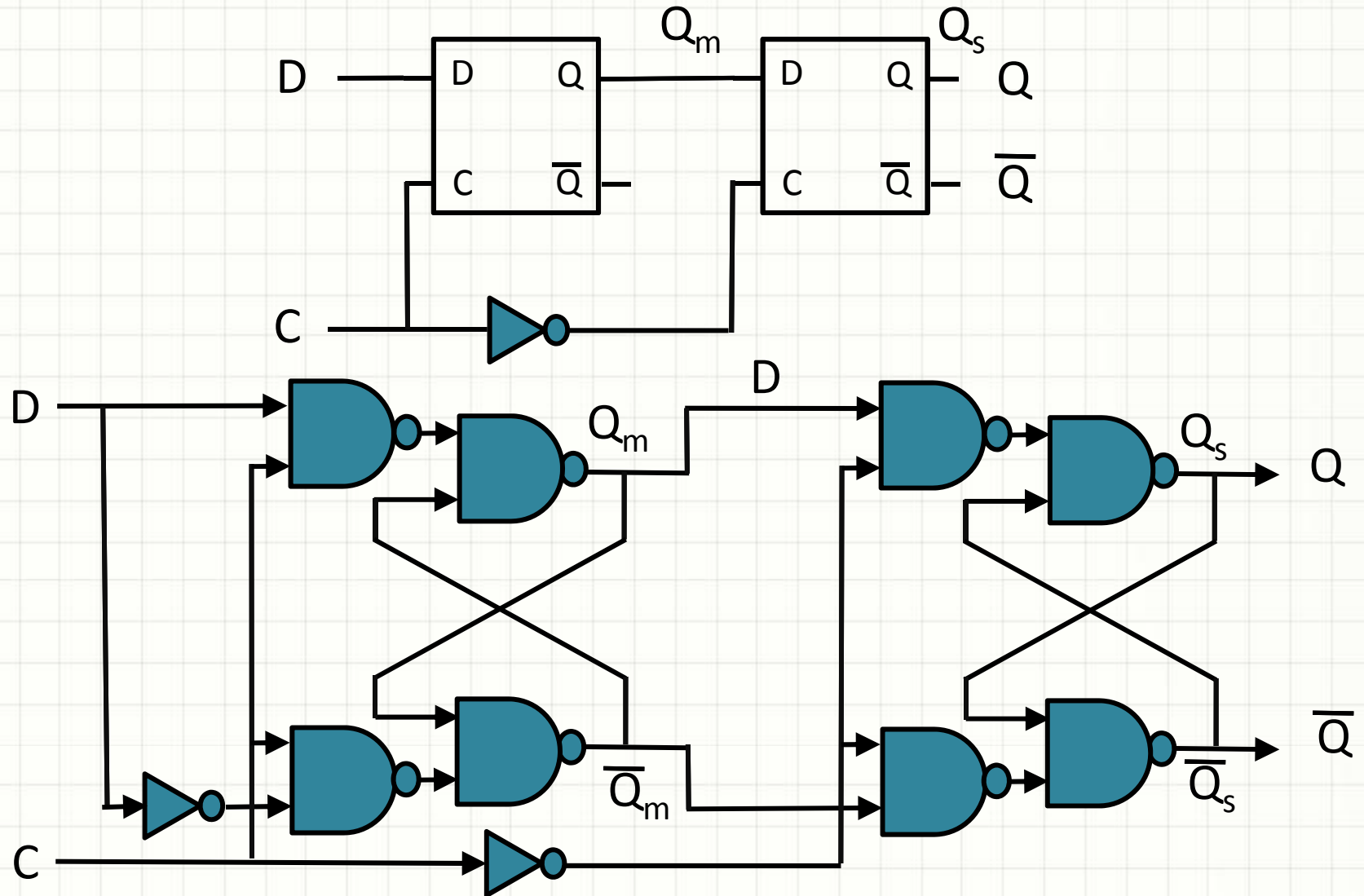


# Edge triggered D Flip-Flop

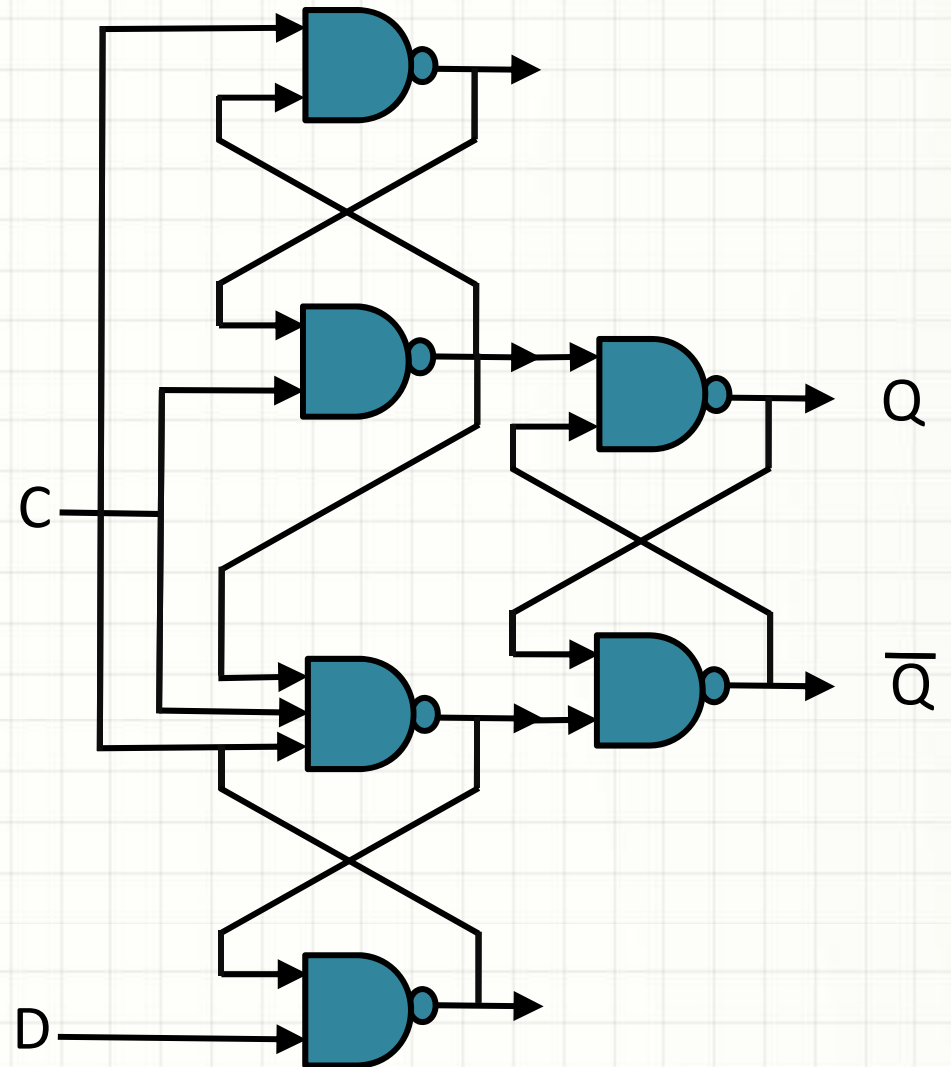 


# Edge triggered D Flip-Flop

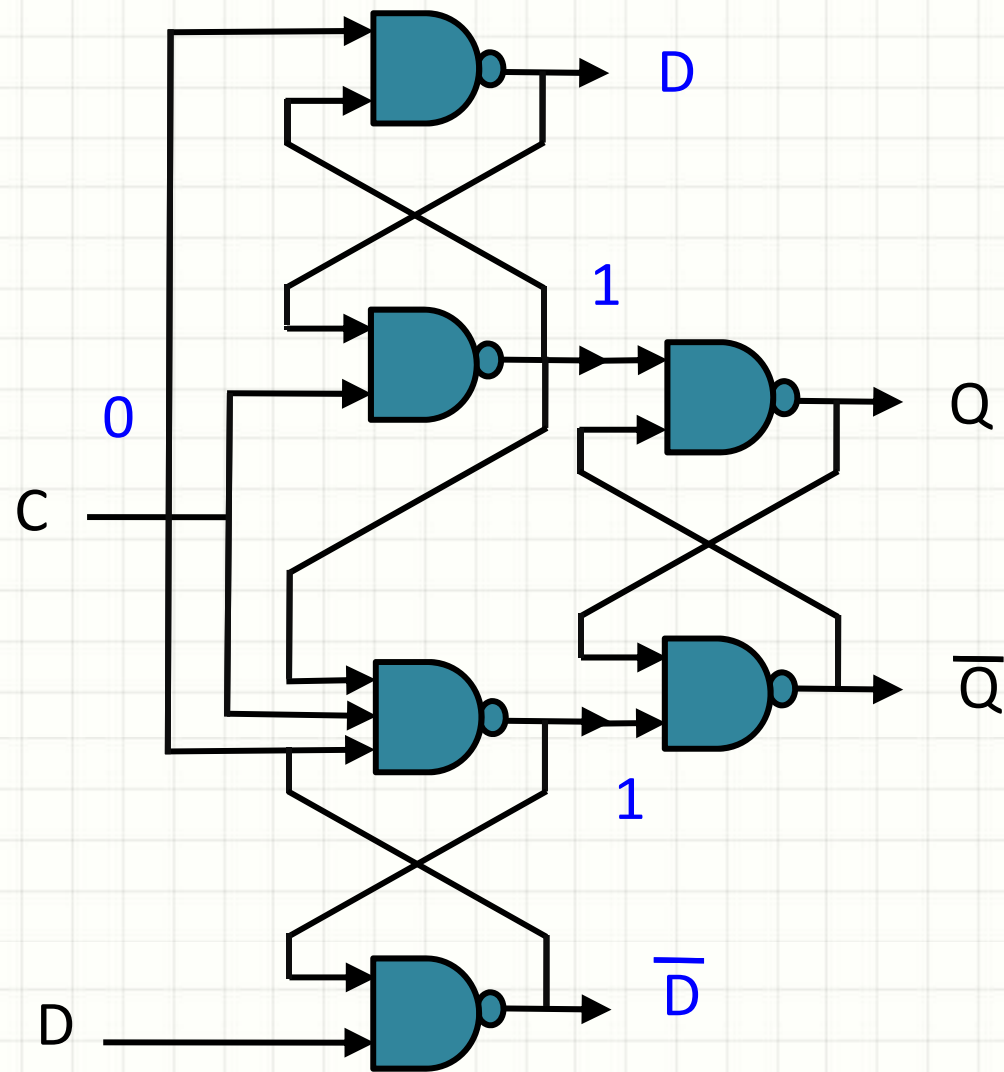


# Edge triggered D Flip-Flop

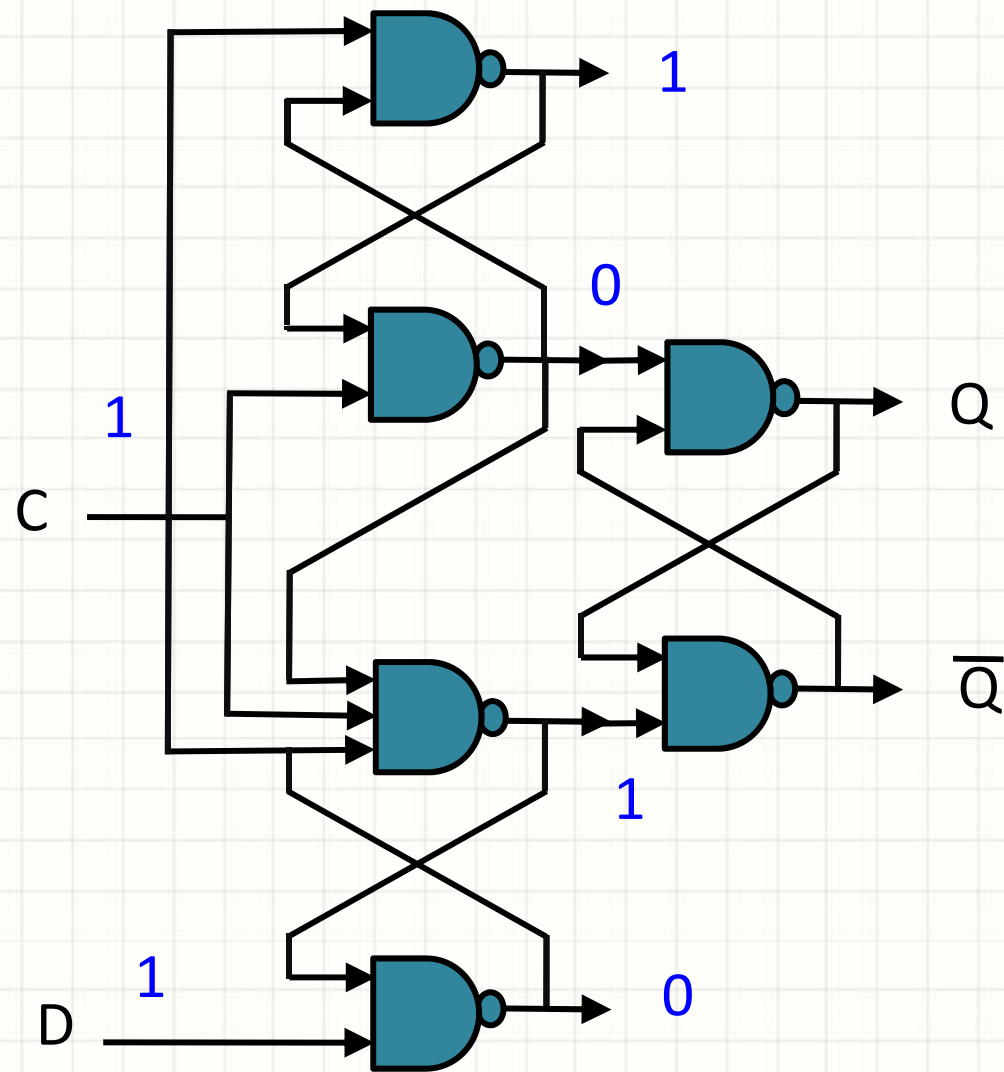


# Edge triggered D Flip-Flop

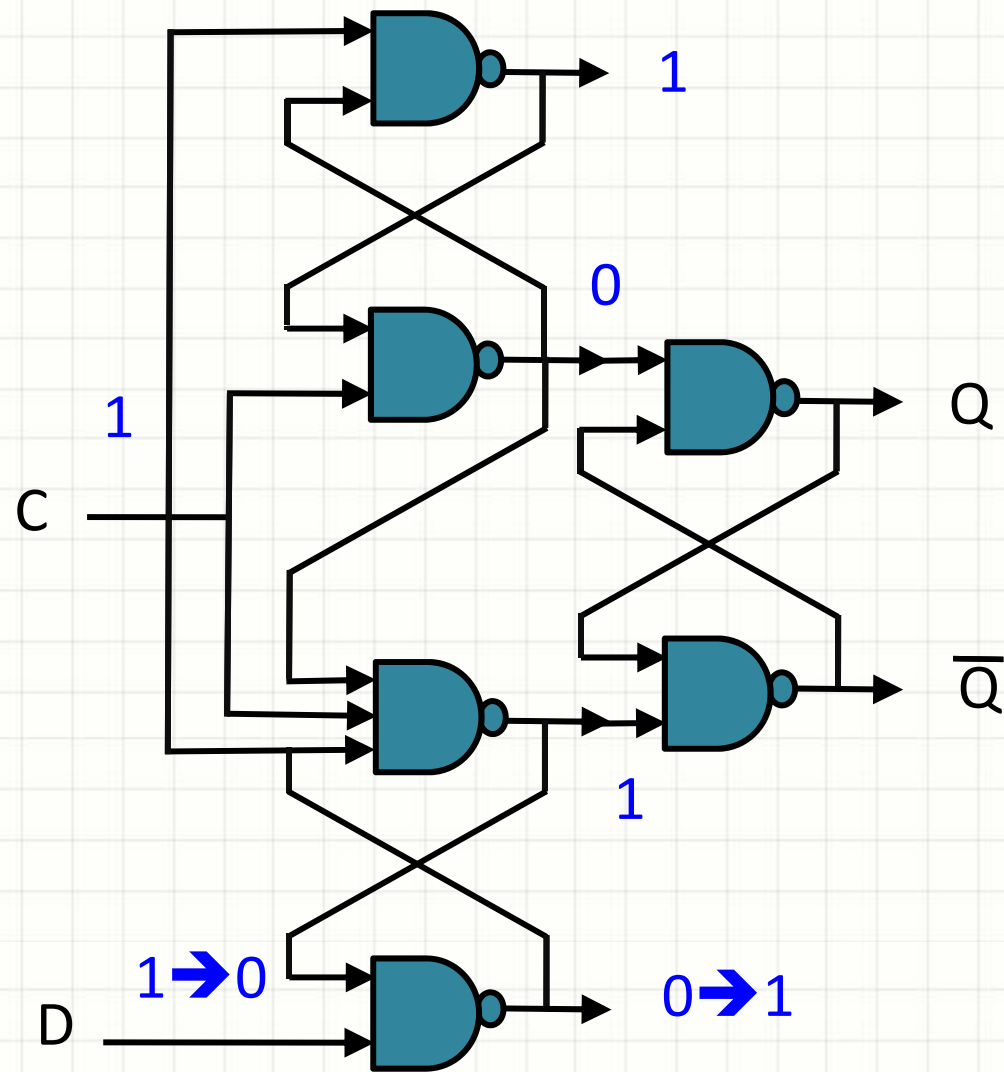

# Edge triggered D Flip-Flop

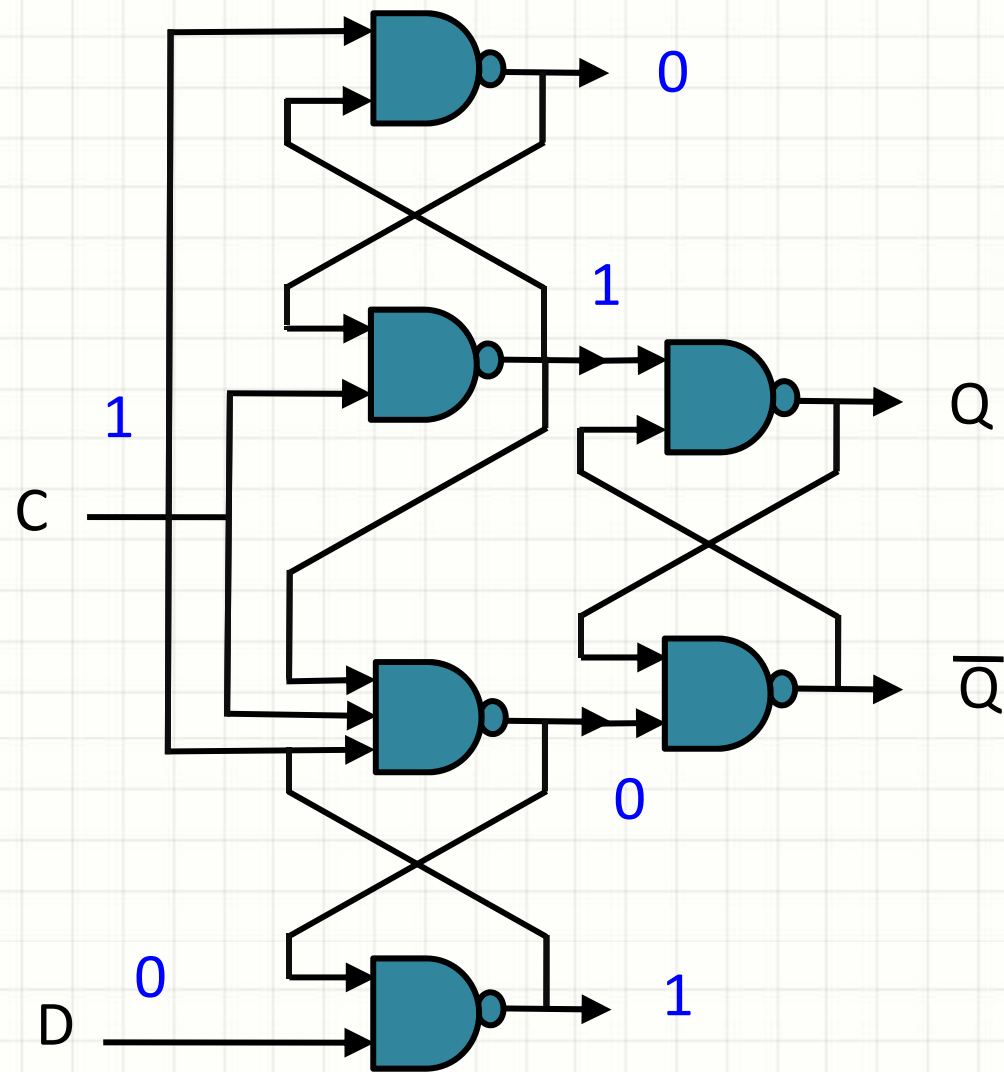

# Edge triggered D Flip-Flop

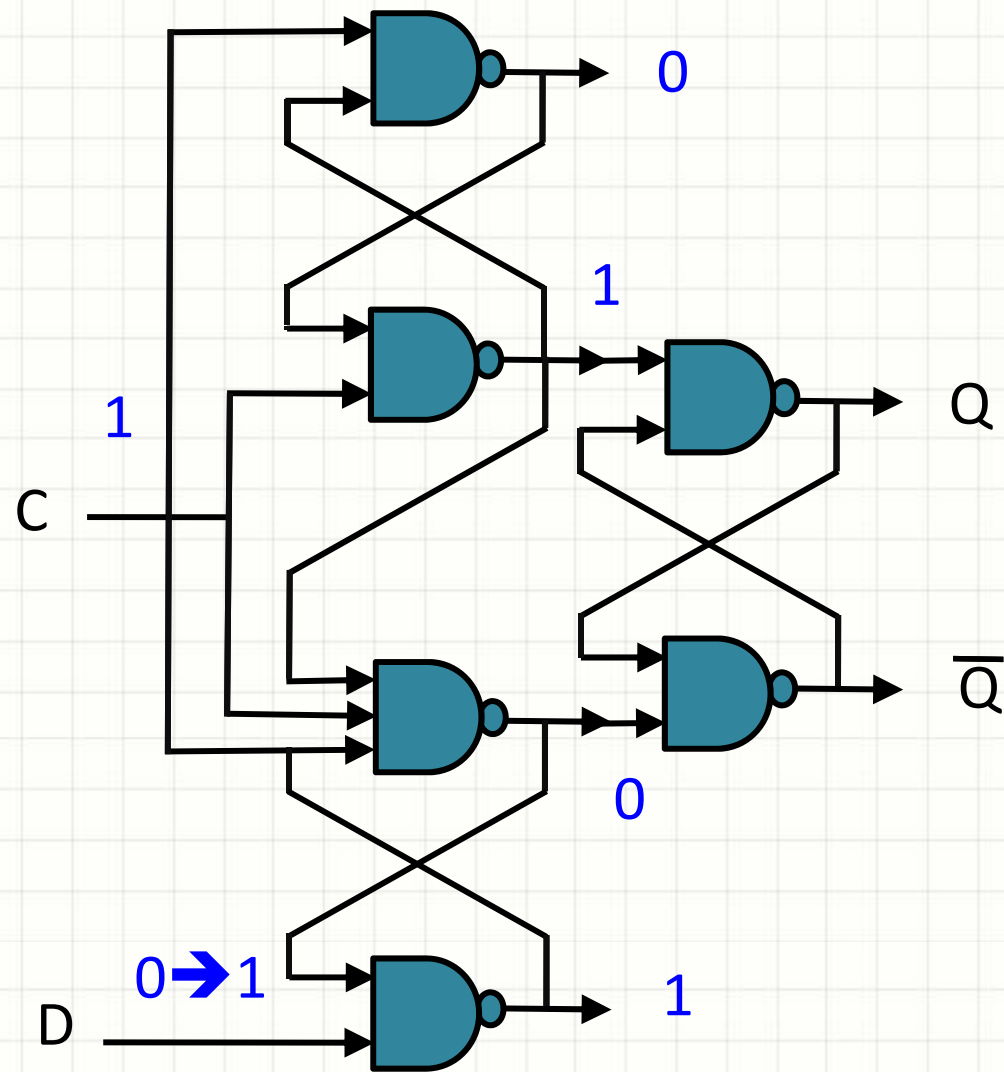





**THANKS**