




COL215 DIGITAL LOGIC AND SYSTEM DESIGN

Testing of Digital Systems
15 November 2017

ATPG


Automatic test pattern generation

 Given a circuit and fault models, determine the test patterns



- Boolean differences
- D-algorithm

Applying Boolean Differences

 

Consider stuck-at fault at e

$$f = Z(a, b, c, e) = a.b + a'.c + e$$

$$dZ/de = Z(a, b, c, e)|_{e=0} \oplus Z(a, b, c, e)|_{e=1}$$

$$= (a.b + a'.c + 0) \oplus (a.b + a'.c + 1)$$

$$= (a.b + a'.c)' = (a' + b') . (a + c')$$

$$= a.b' + a'.c' + b'.c'$$

Test vector for e/0 satisfies –

$$dZ/de . e = (a.b' + a'.c' + b'.c') . e$$

$$= (a.b' + a'.c' + b'.c') . (b.c) = 0$$


Test vector for e/1 satisfies –

$$dZ/de . e' = (a.b' + a'.c' + b'.c') . e'$$


$$= (a.b' + a'.c' + b'.c') . (b' + c')$$

$$= a.b' + a'.c' + b'.c'$$


Applying D Algorithm

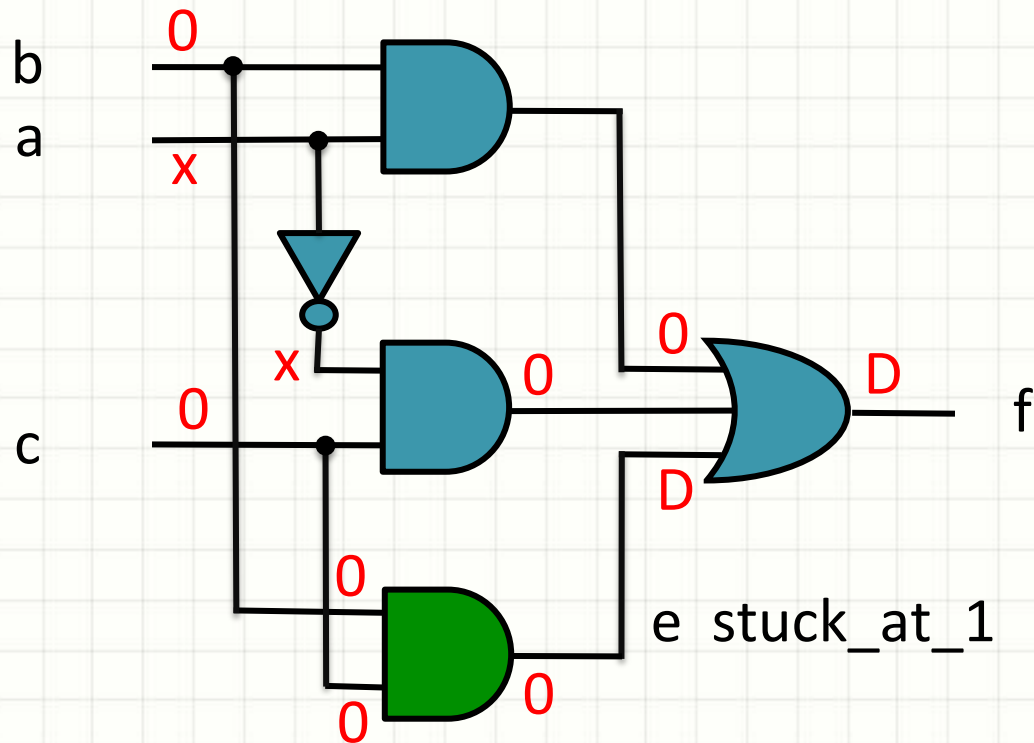


Applying D Algorithm

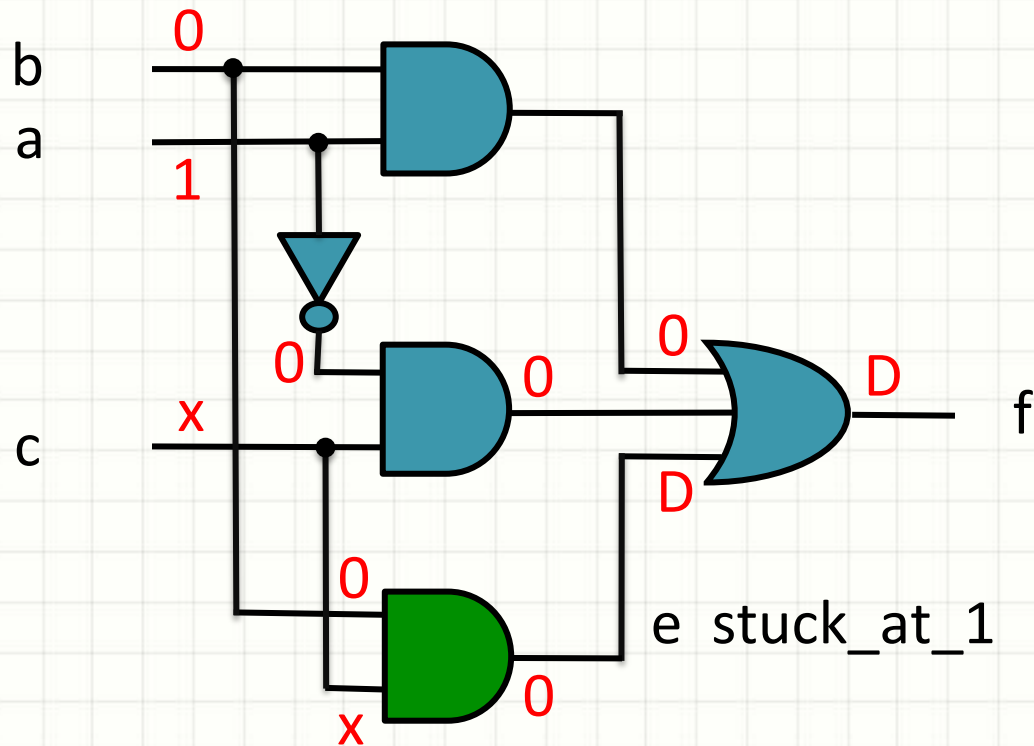


Applying D Algorithm

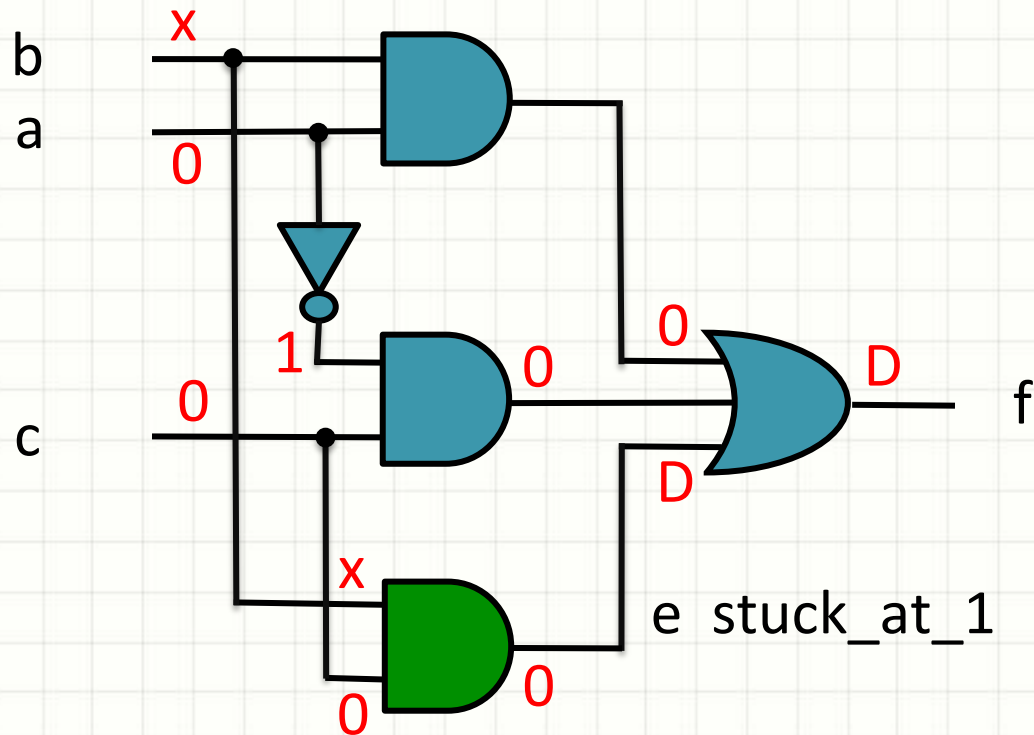


Applying D Algorithm

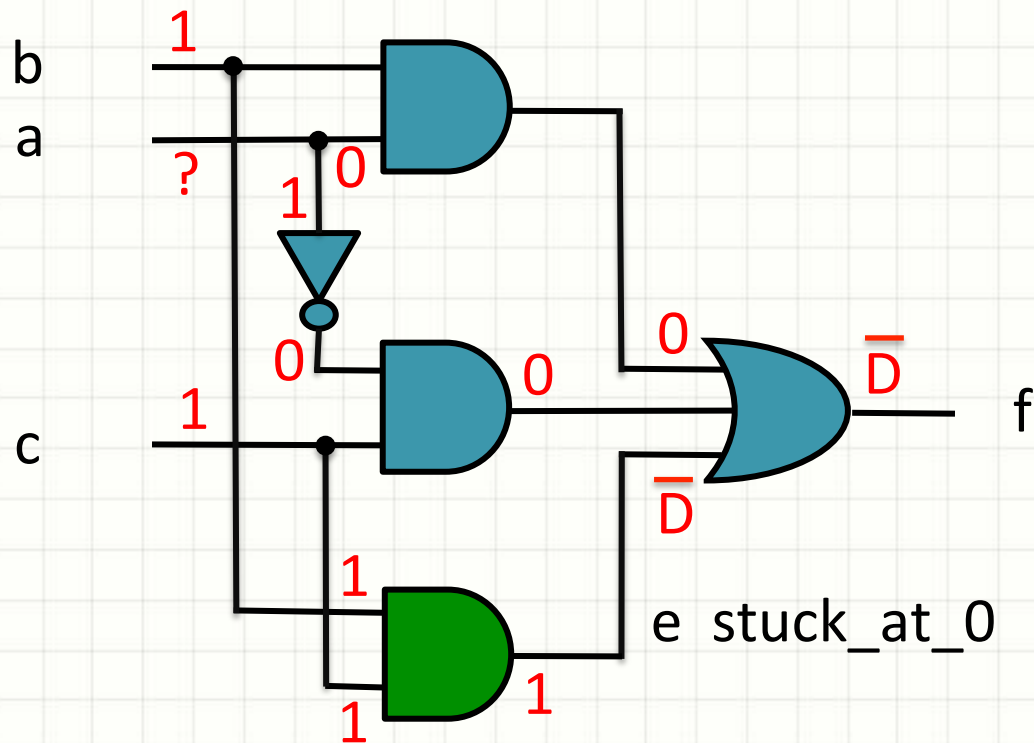


Applying D Algorithm

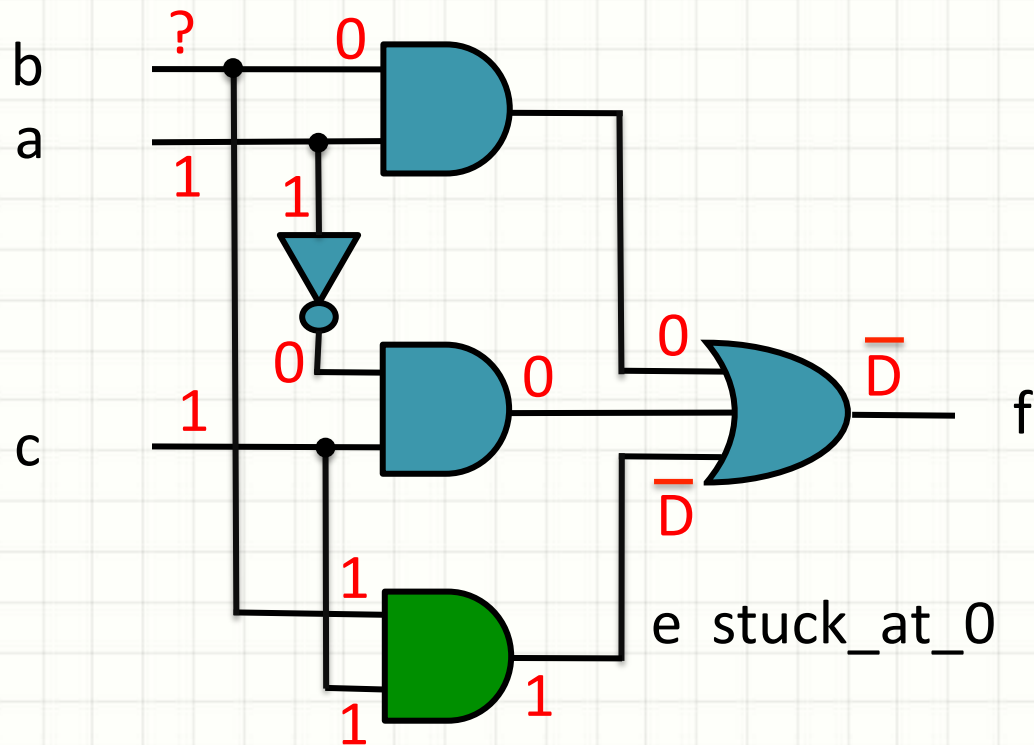

Applying D Algorithm

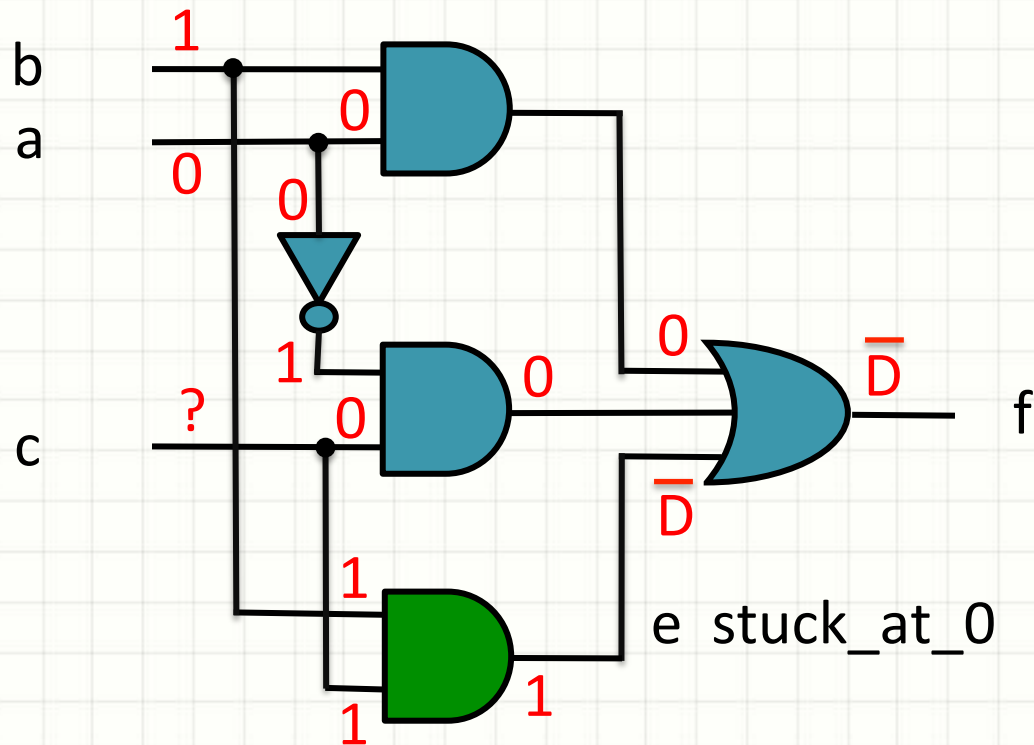


Testing of sequential circuits

 

- How do you know the present state?
- Can you test just by applying inputs and observing outputs?

Testing of sequential circuits

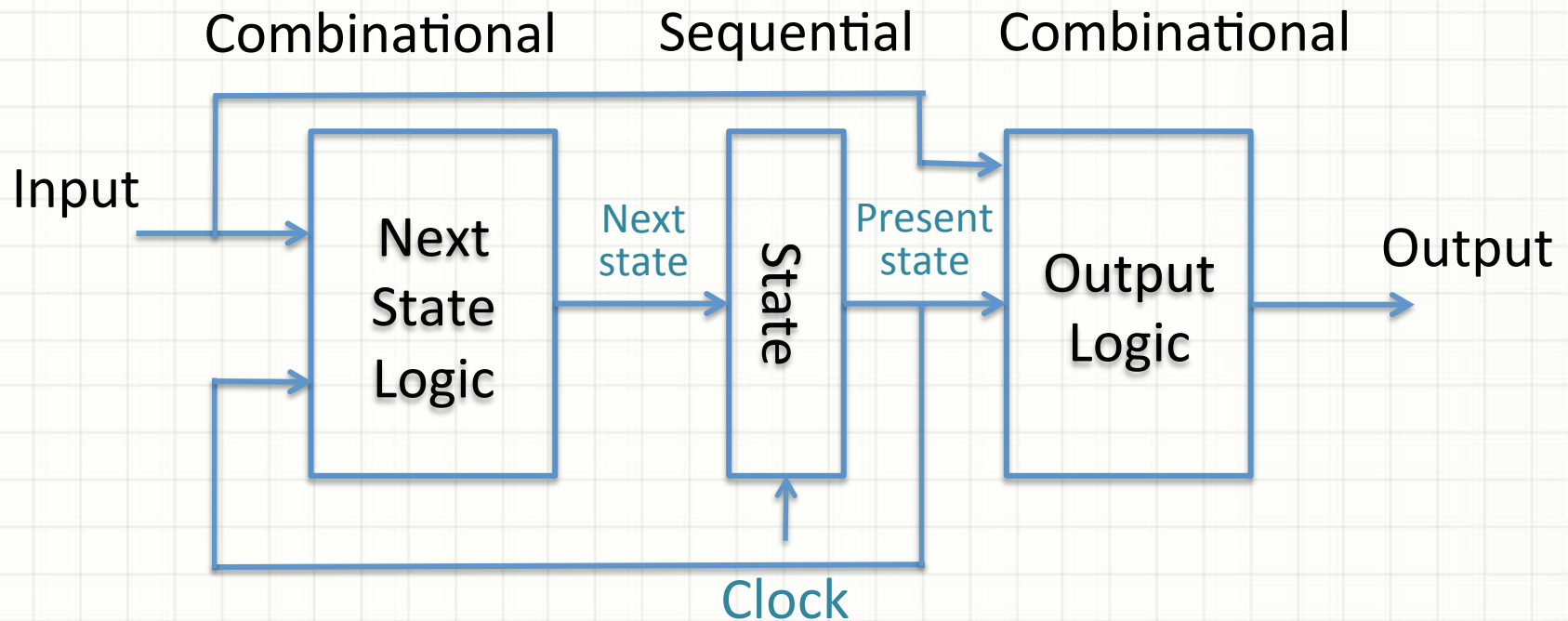

- Useful to have a reset input for the state register to take the FSM to a known initial state
- Test transitions from initial state to other states
- Test other state transitions and outputs

Testability

Defined in terms of

- controllability: ease /difficulty of setting a particular logic signal to a 0 or a 1
 - primary inputs are always controllable
 - other signals may be controlled through primary inputs
- observability: ease /difficulty of observing the value of a logic signal
 - primary outputs are always observable
 - other signals may be observed through primary outputs

Design for Testability (DFT)

Making a design more testable


- Adhoc DFT
 - "good" design practices or guidelines
- Structured DFT
 - involves adding extra logic and signals dedicated for test according to some procedure

Adhoc DFT


- Avoid *asynchronous* logic feedbacks.
 - Feedback can result in oscillation.
 - ATPG are designed to work on acyclic combinational logic.
- Make FFs initializable, i.e., provide clear and reset.
- Avoid gates with a large fan-in.
 - Large fan-in makes the inputs difficult to observe and the output difficult to control.
- Provide test control for difficult to control signals.
 - For example, signals produced by a long counter require many clock cycles to control.
 - This increases the length of the test sequence.

Structured DFT

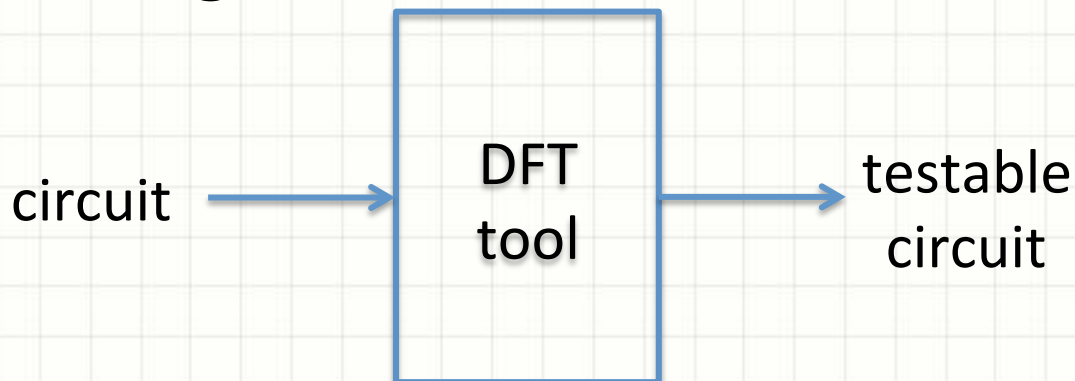
- Add extra logic and signals dedicated for test according to some procedure
- Scan based DFT is the most common approach
- Tools exist to carry out this modification of the designs



Design for testability - scan

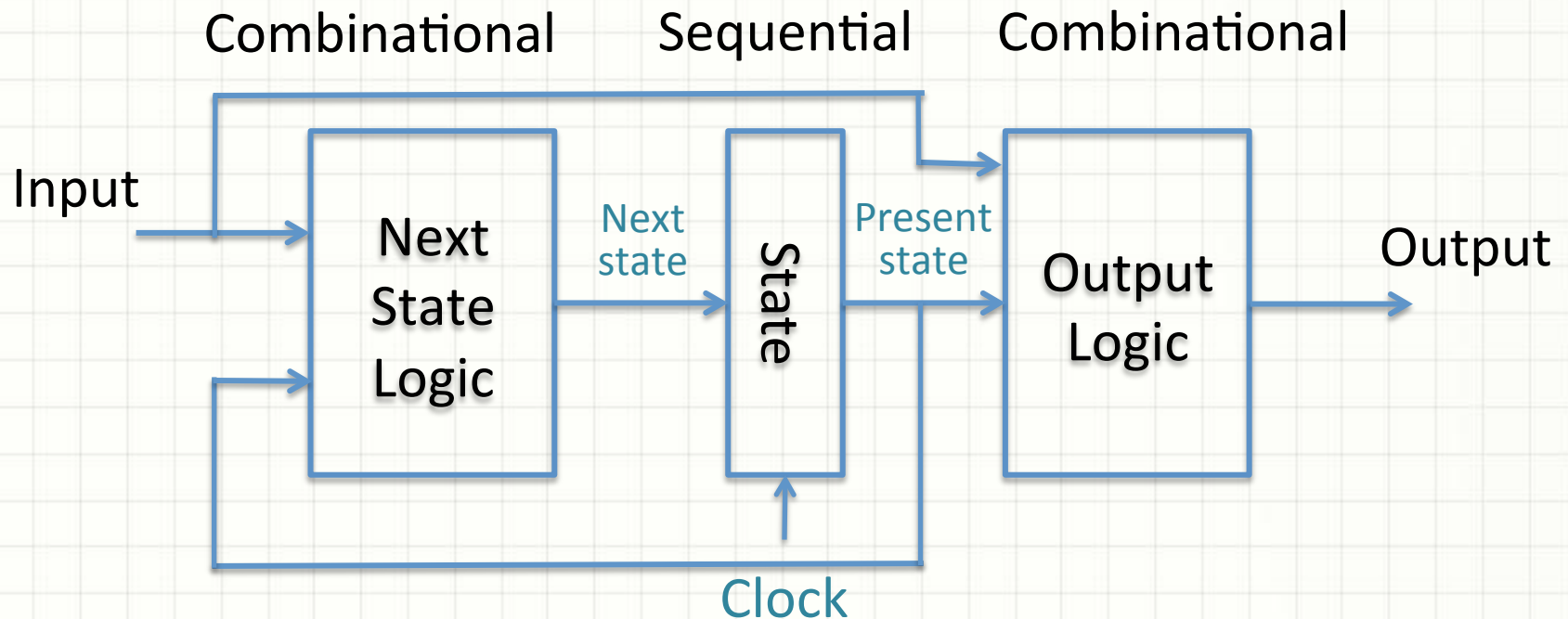

Design for testability - scan

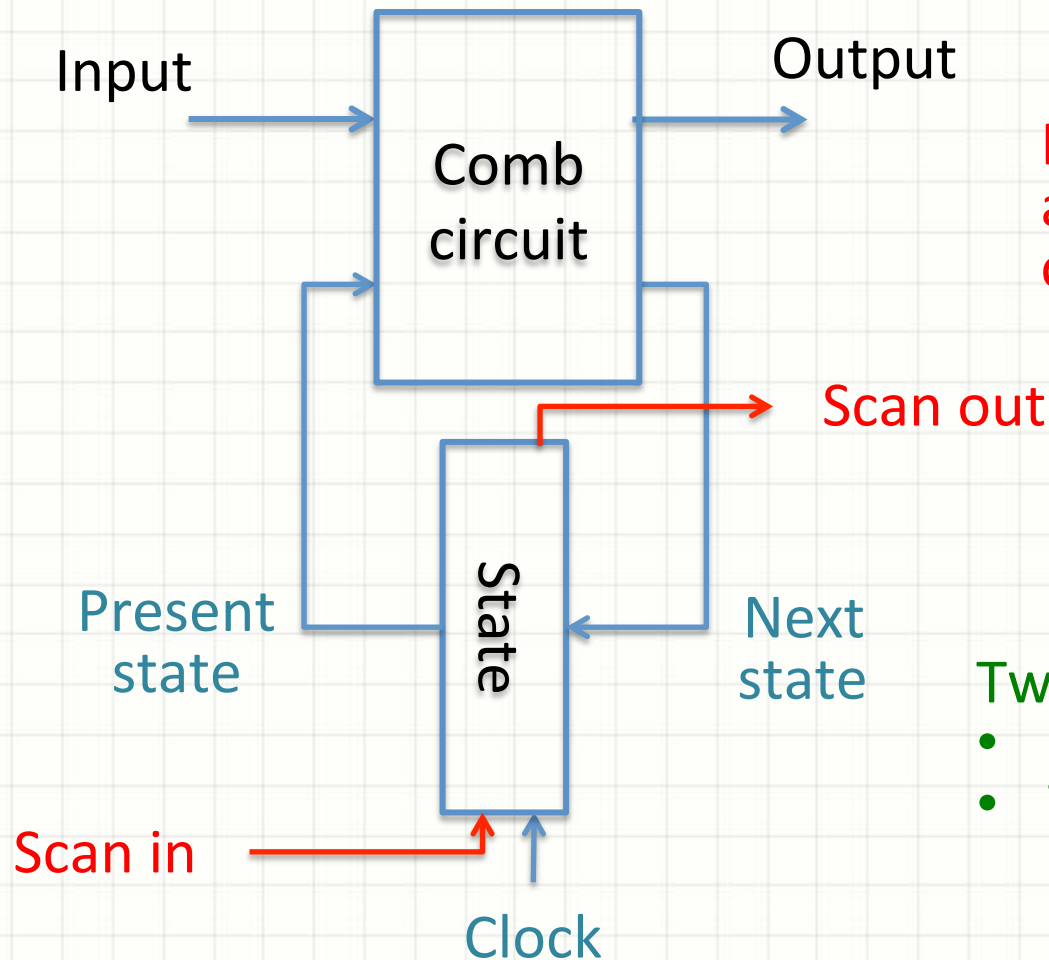

Improve controllability
and observability
of the state register

Two modes of operation:

- Normal mode
- Test mode


Scan variations

- Full scan | partial scan
- Single scan chain | multiple scan chains
 - more test time vs more input/output pins


Built-in Self Test (BIST)

- Test patterns are generated internally
- No need to deal with large volumes of test data.
- It can be used to perform *at-speed* test.
- BIST entails three tasks:
 - TPG
 - Test application
 - Response verification
- Our focus on Logic BIST not Memory BIST

BIST

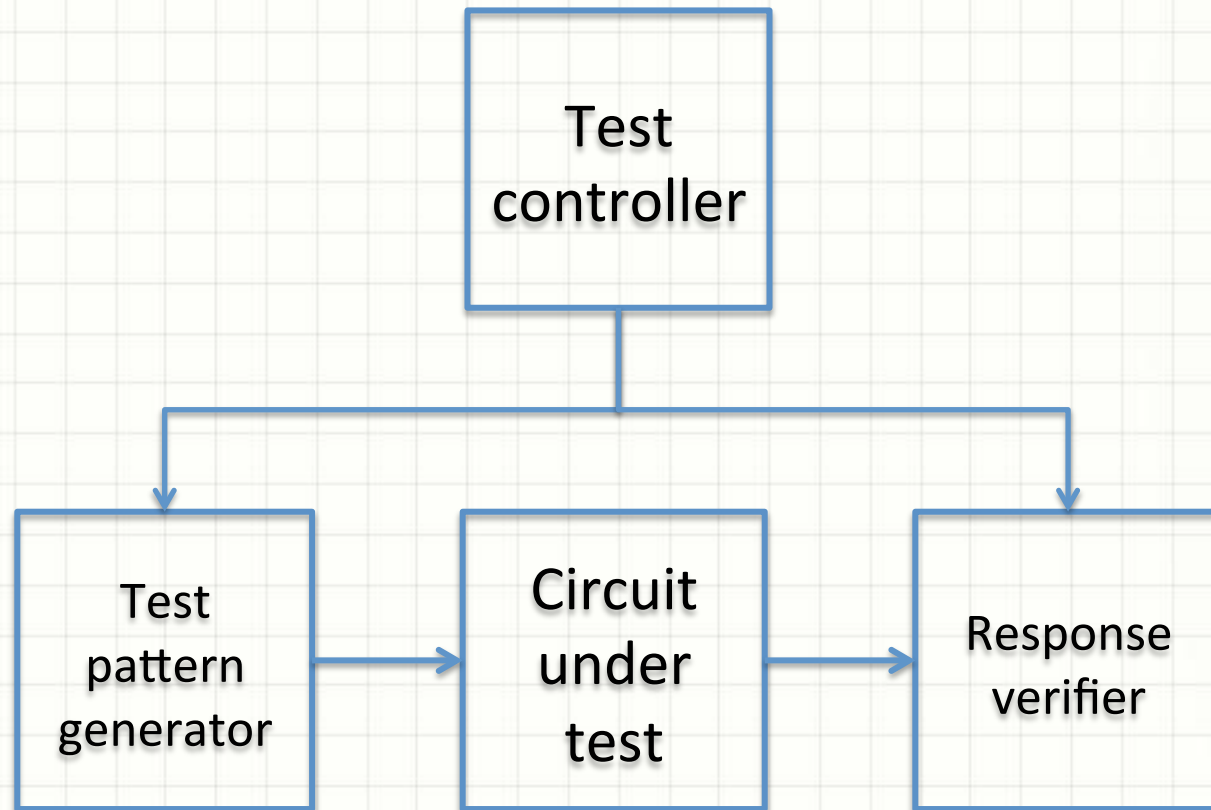

Pseudo random sequence generator (PRSG)

 

1 0 0 0

1 1 0 0

1 1 1 0

1 1 1 1

0 1 1 1

1 0 1 1

0 1 0 1

1 0 1 0

1 1 0 1

0 1 1 0

0 0 1 1

1 0 0 1

0 1 0 0


0 0 1 0

0 0 0 1

1 0 0 0

Linear Feedback
Shift Register (LFSR)

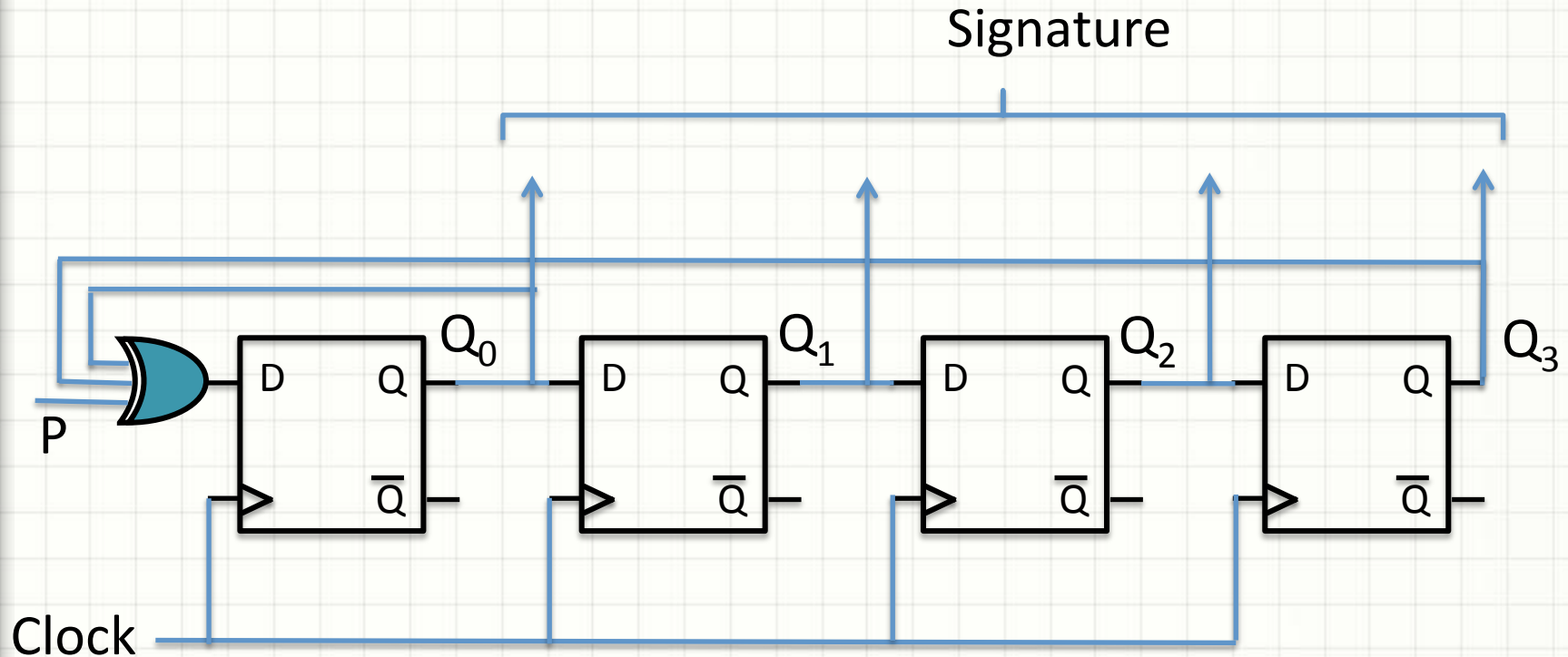Input compressor circuit/ Signature analyser



- Single input and multiple input compressors
- BILBO: Built-in logic block observer
 - combines scan, TPG, SA

What have we learnt?

- Logic design (combinational circuits)
 - truth tables, expressions, circuits, minimization
- Logic design (sequential circuits)
 - state transition tables, diagrams, state minimization
- Combinational & sequential modules
 - mux/demux, coders/decoders, FFs, registers, counters
- From logic to arithmetic
 - representations, conversions, operations and operators

What have we learnt?

- Technology
 - transistor to FPGA and things in between
- Design
 - VHDL: data flow, procedural, structural
 - from algorithmic description to circuits
 - control-data partition
- Testing
 - testing tools, design for testability



THANKS