



COL215 DIGITAL LOGIC AND SYSTEM DESIGN


Sequential Circuits

02 August 2017


Lecture Outline

- Basic memory elements
- Gated latches
- Master-Slave flip-flops
- Edge triggered flip-flops

A simple storage element

 


A simple storage element

 

How to change the stored value?


A Set-Reset Latch (SR Latch)

 

R : Reset


S : Set

SR Latch redrawn

 


S	R	Q_a	Q_b

SR Latch redrawn

 


S	R	Q _a	Q _b
0	1	0	1
1	0		

SR Latch redrawn

 


S	R	Q _a	Q _b
0	0		
0	1	0	1
1	0	1	0

SR Latch redrawn

 

S	R	Q _a	Q _b
0	0		
0	1	0	1
1	0	1	0


SR Latch redrawn

 


S	R	Q _a	Q _b
0	0	0/1	1/0
0	1	0	1
1	0	1	0
1	1		

Don't allow $S = 1$ as well as $R = 1$
or allow above, but allow only
one input change at a time


Gated SR Latch

 


C	S	R	Q (t+1)
0	-	-	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


Gated SR Latch using NAND gates

 


C	S	R	$Q(t+1)$
0	-	-	$Q(t)$
1	0	0	$Q(t)$
1	0	1	0
1	1	0	1
1	1	1	?

 


D Latch

 



C	D	$Q(t+1)$
0	-	$Q(t)$
1	0	0
1	1	1

 



D Latch (D changes while C = 1)

 

C	D	$Q(t+1)$
0	-	$Q(t)$
1	0	0
1	1	1

  

Master-Slave D Flip-Flop

  



QUESTIONS?