




COL215 DIGITAL LOGIC AND SYSTEM DESIGN


Real Circuits :
Transistors and Gates
continued

20 September 2017

I/O characteristics of CMOS inverter

 


Noise Margin

 


$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

Dynamic operation and delays


 


Power dissipation in CMOS inverter

 


$$\text{power} = f C V_{DD}^2$$

  Using NMOS / PMOS transistors as switches




Passing 1's through NMOS switch

Passing 0's through PMOS switch

 

 
$V_{GS} = V_{DD} - V_A$
Transistor cuts off if
 V_A rises above $V_{DD} - V_T$




$V_{GS} = 0 - V_B$
Transistor cuts off if
 V_B falls below V_T

Passing 0's through NMOS switch

Passing 1's through PMOS switch

 


Transistor remains ON
 V_A is 0

 

Transistor remains ON
 V_B equals V_{DD}

Fan-in limitation

 


Effective channel length = $k \cdot L$

⇒ increased delay
increased V_{OL}

This limits the fan-in


Higher fan-in in CMOS

Fan-out limitation

 


Increased load capacitance

⇒ increased delay
slower rise / fall

 


Simple buffer

$$y = x$$

 



designed to drive
large loads

 

symbol


Tri-state buffer

e	x	y
0	0	Z
0	1	Z
1	0	0
1	1	1

  


symbol

Transmission Gate

 


Same truth table as
tri-state buffer

 


symbol

Multiplexer

 

Ex-OR Gate

 



THANKS