



COL215 DIGITAL LOGIC AND SYSTEM DESIGN

Adders and Multipliers in FPGA

29 September 2017

FPGA Manufacturers



First FPGA device in 1984
EPROM based



First FPGA device in 1985
SRAM based



Anti fuse based



Xilinx FPGA Portfolio

45nm

SPARTAN⁶

28nm

VIRTEX⁷

KINTEX⁷

ARTIX⁷

SPARTAN⁷

20nm

VIRTEX⁷
UltraSCALE

KINTEX⁷
UltraSCALE

16nm

VIRTEX⁷
UltraSCALE+

KINTEX⁷
UltraSCALE+

XC2064 : 64 CLBs, 56 IOBs, 18 MHz

XC7A35T-1CPG236C : 5200 slices, 236 pins, 464 MHz
90 DSPs, 1800 KB RAM

XC7VX1140T : 178,000 slices, 1100 pins, 540-740 MHz
3,360 DSPs, 67,680 Kb RAM


Xilinx Spartan 6 FPGA

- Configurable Logic Blocks (CLBs)
- DSP48A1 slices
- Block RAMs
- DRAM controllers
- Clock Management Tiles (CMTs)
- Input/Output interfaces


Types of slices

Feature	SLICEX	SLICEL	SLICEM
6-Input LUTs	√	√	√
8 Flip-flops	√	√	√
Wide Multiplexers		√	√
Carry Logic		√	√
Distributed RAM			√
Shift Registers			√

Fast Carry Chain

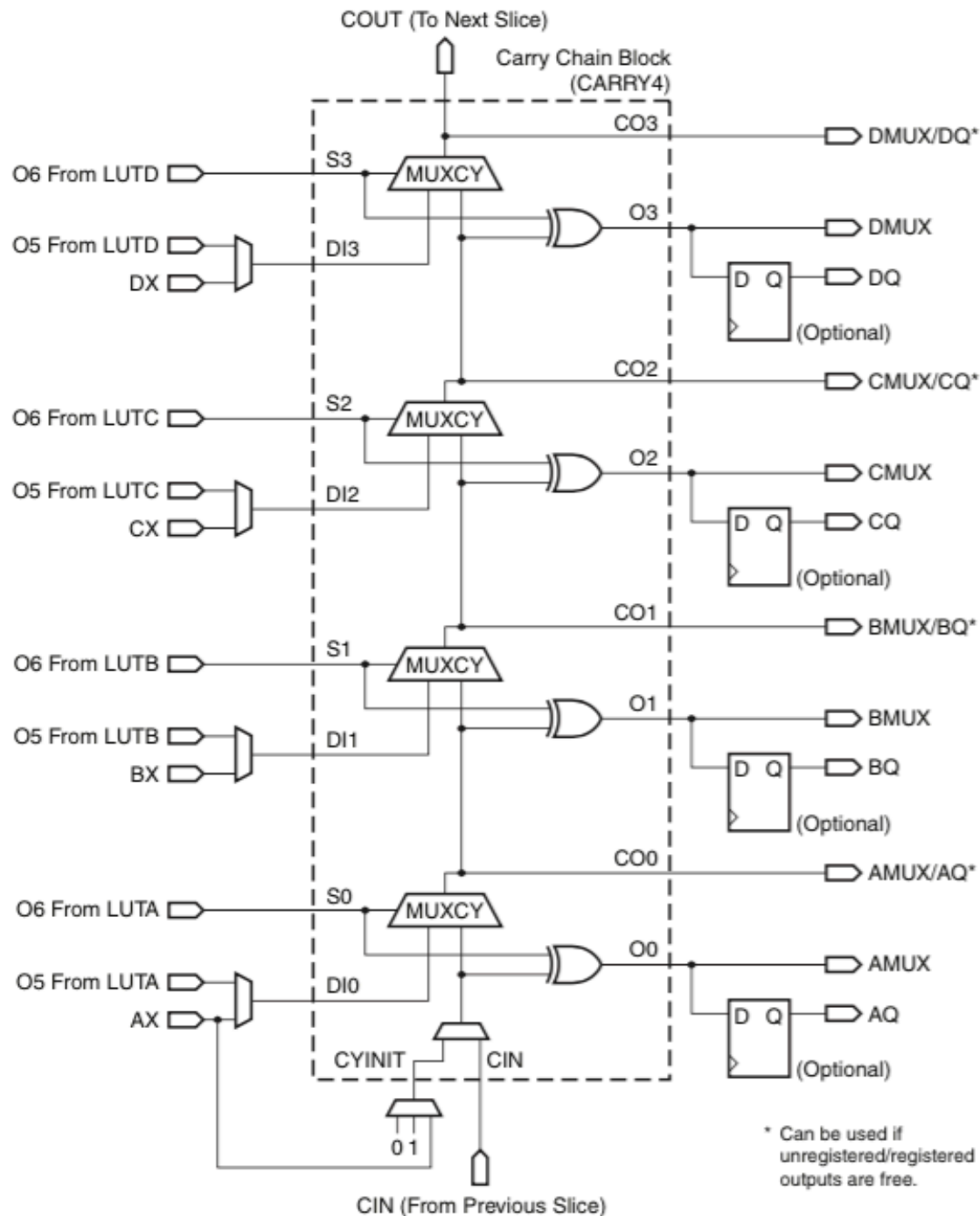

Fast Carry Chain

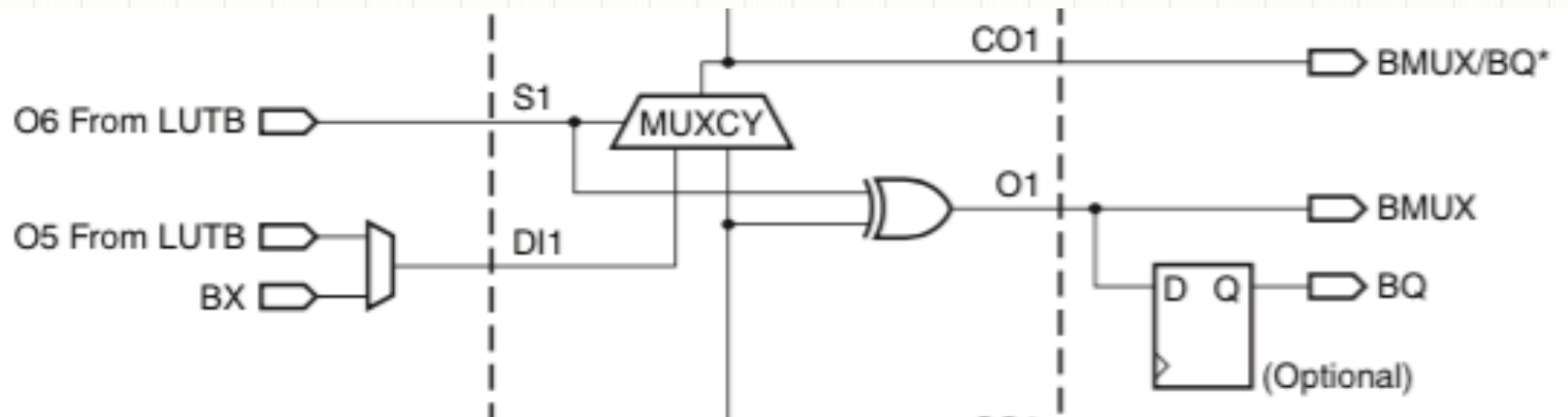


Xilinx Spartan 6 FPGA

- Configurable Logic Blocks (CLBs)
- DSP48A1 slices
- Block RAMs
- DRAM controllers
- Clock Management Tiles (CMTs)
- Input/Output interfaces


DSP48A1 Slice

- 48 bit add / subtract
- 18 x 18 multiplication with 36 bit product
- Designed for multiply-accumulate operations
- Pipelined operation possible
- Multiple modules can be cascaded for larger data sizes


Block diagram

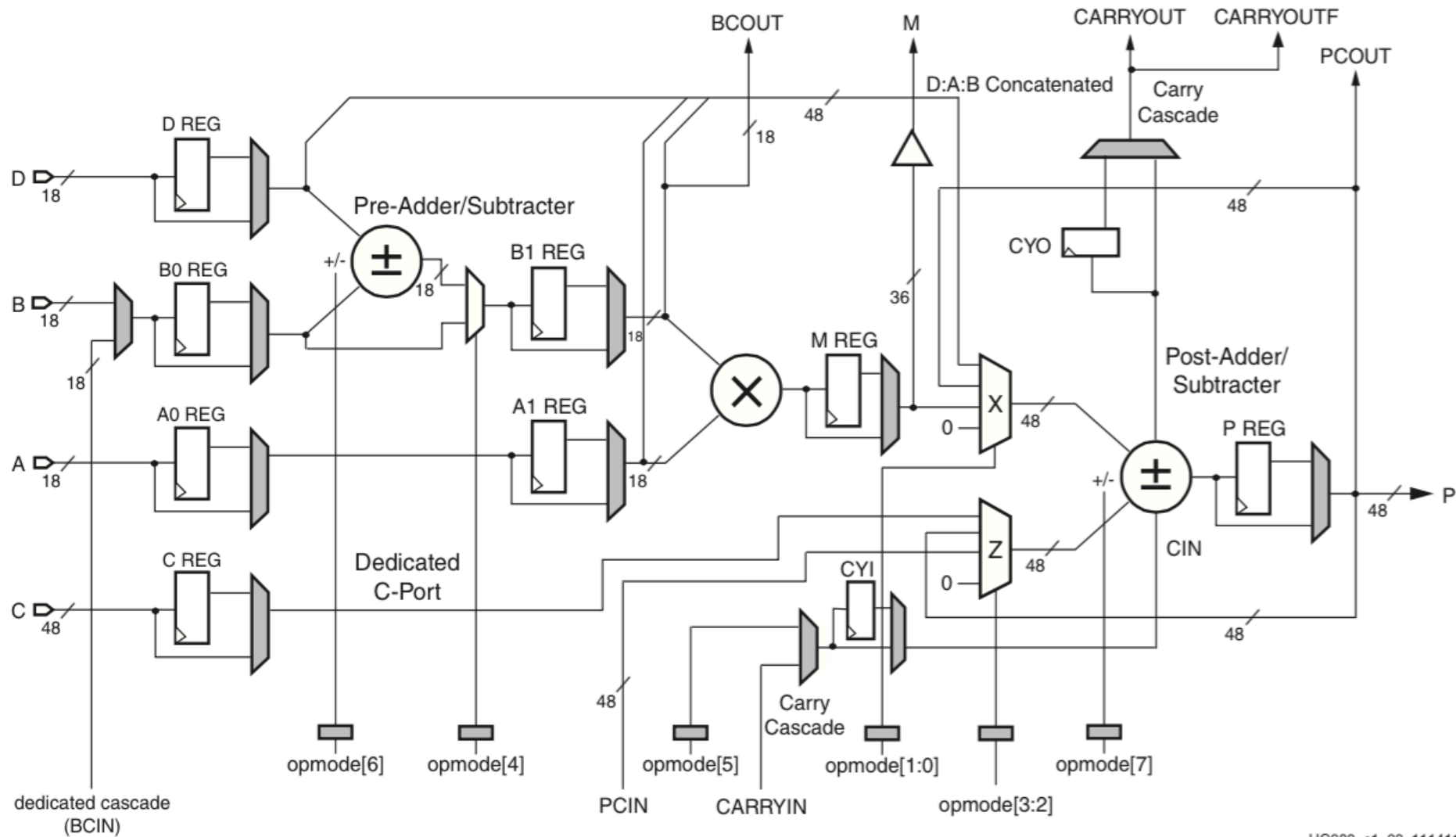


Simplified block diagram

 


Accumulation function

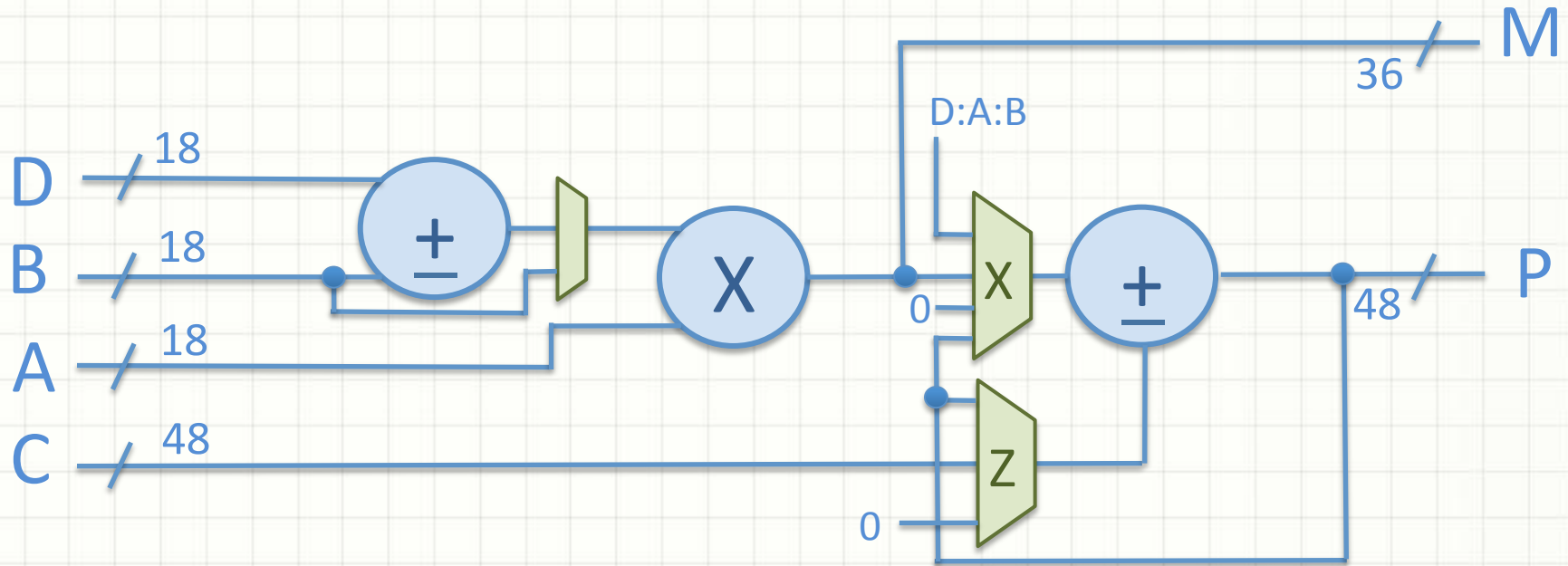


Pipelining registers

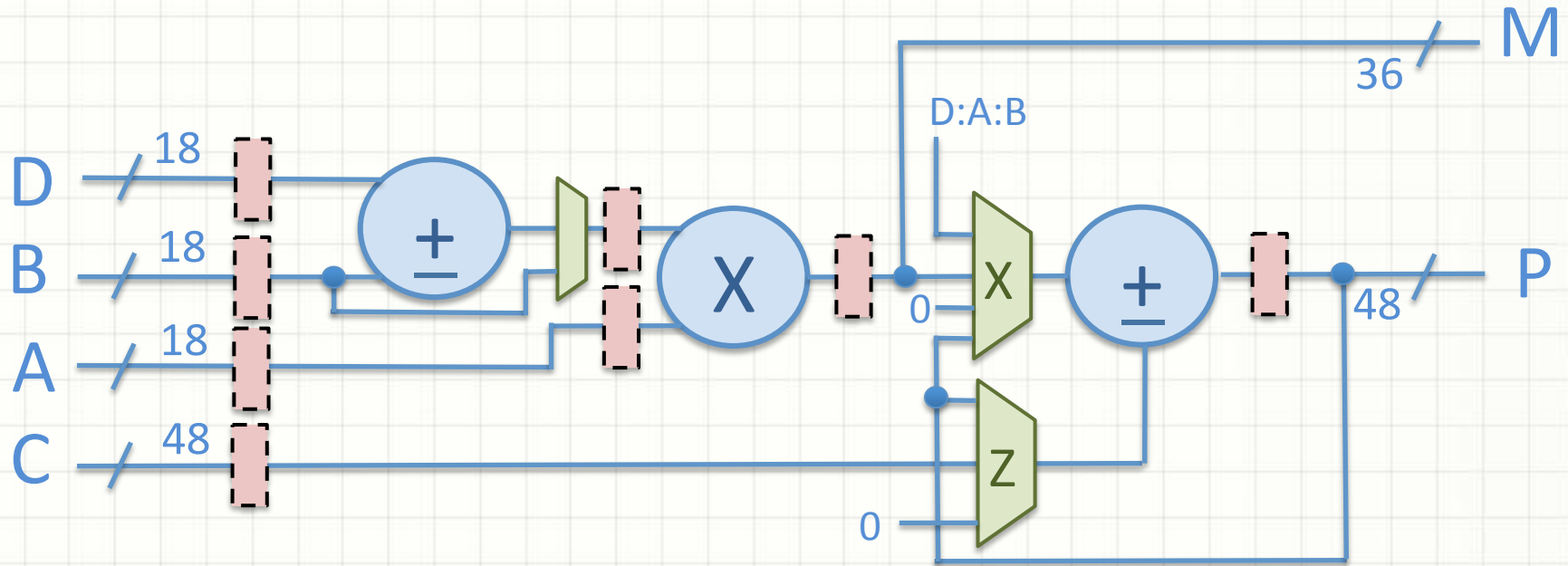

Register configuration

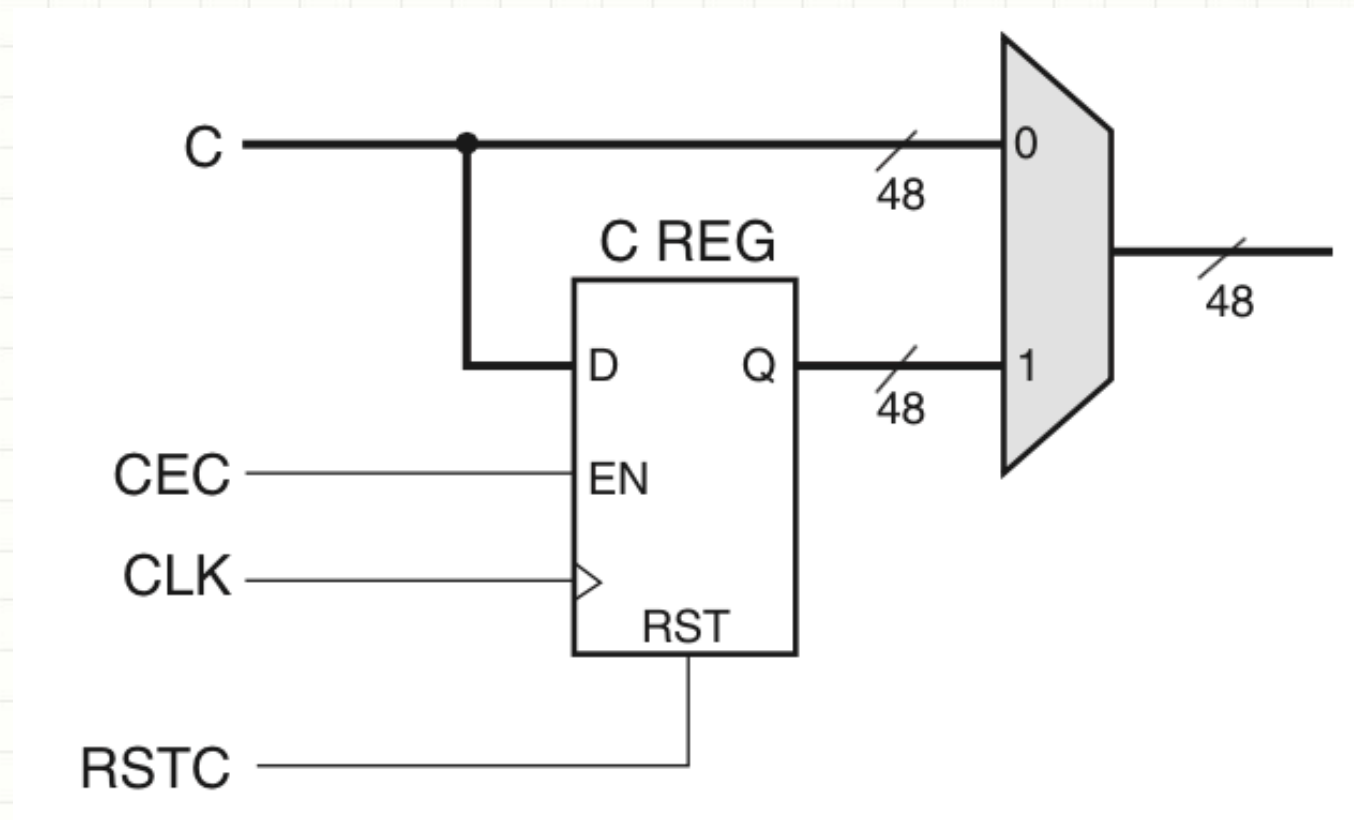


Control

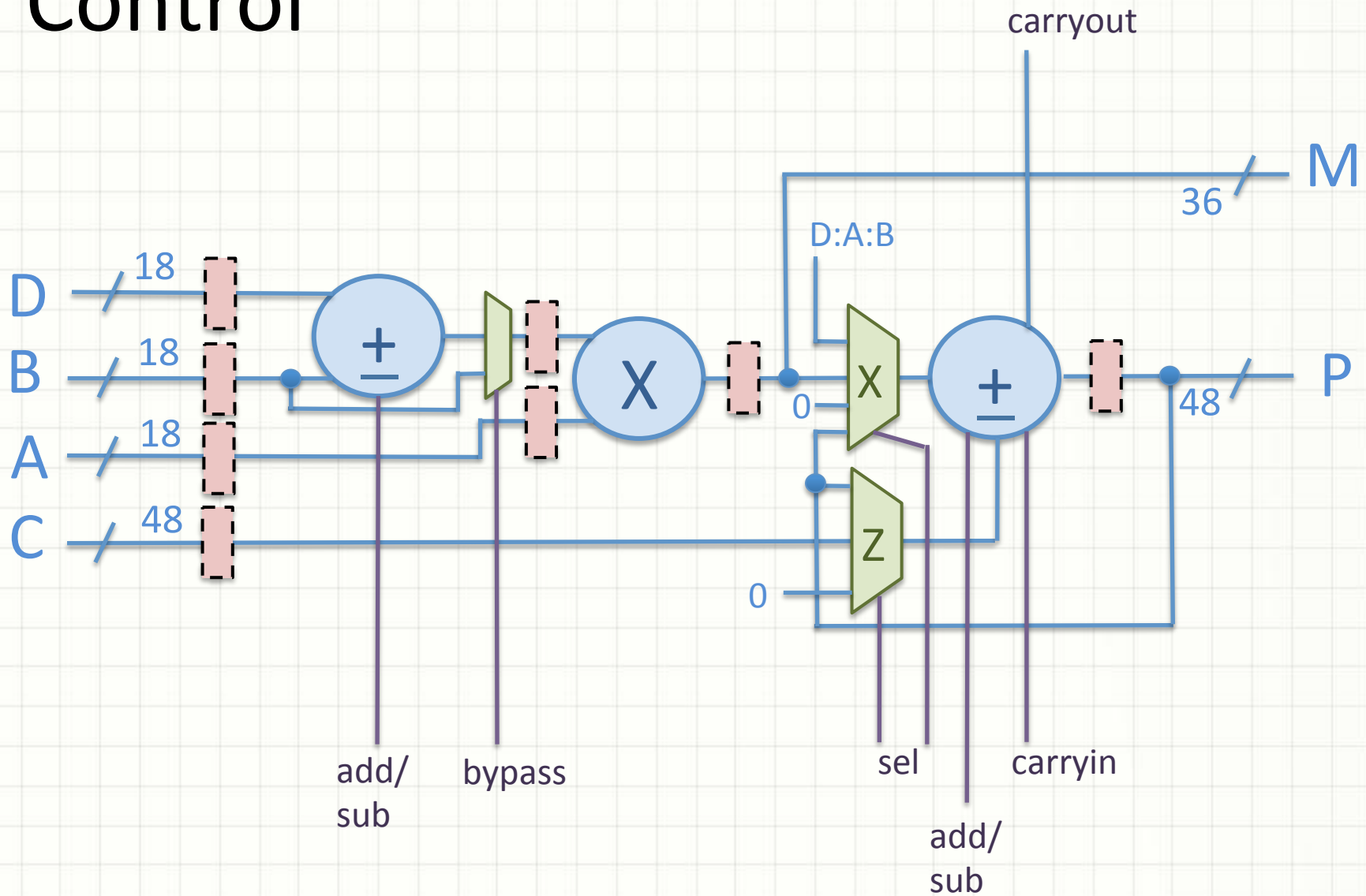


Computing weighted sum

- $s = w_0 \times a_0 + w_1 \times a_1 \dots w_{n-1} \times a_{n-1}$
 - Weights : w_i
 - Data values : a_i
- Common operation in
 - digital signal processing
 - digital image processing
(filtering, convolution, correlation, spectrum computation, . . .)


Block diagram

 


Block by Block Computation

 


Computation with sliding window

 

 
Weights in memory, Data streamed in, Sum streamed out




Weights, Data and Sum, all in memory

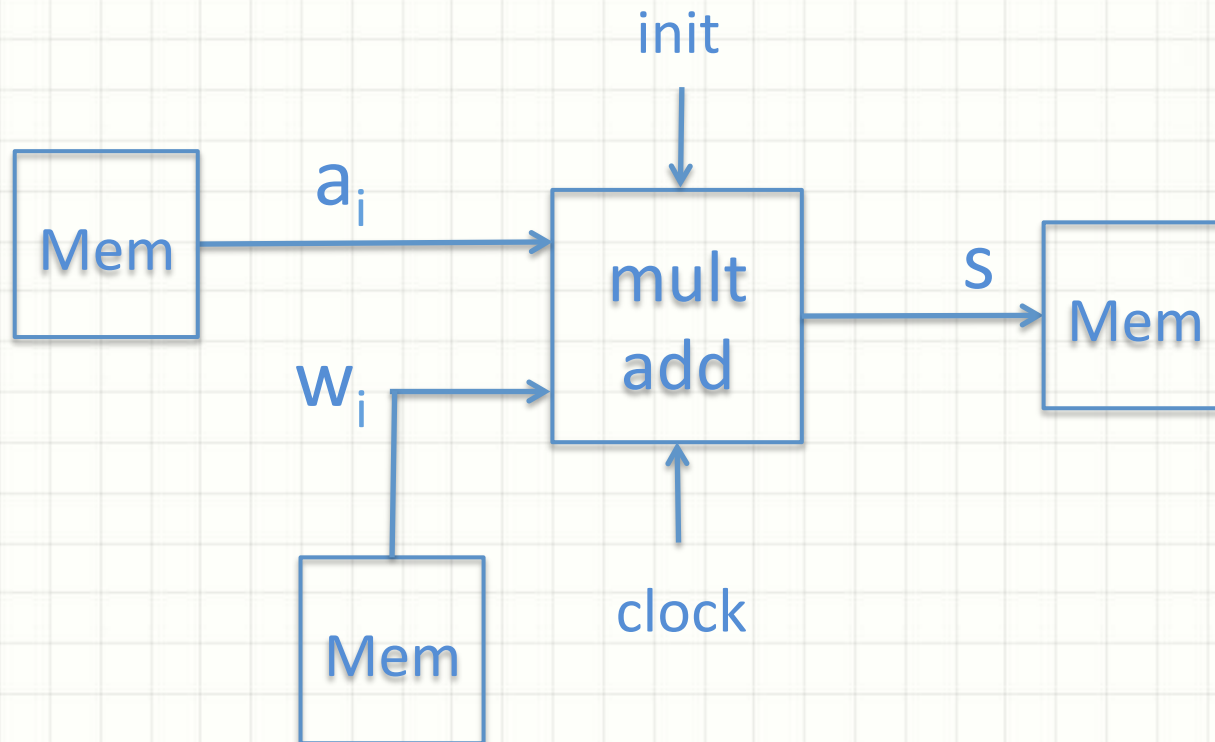

Weighted sum implementation

 


Timings

 


Weighted sum implementation


Introduce registers

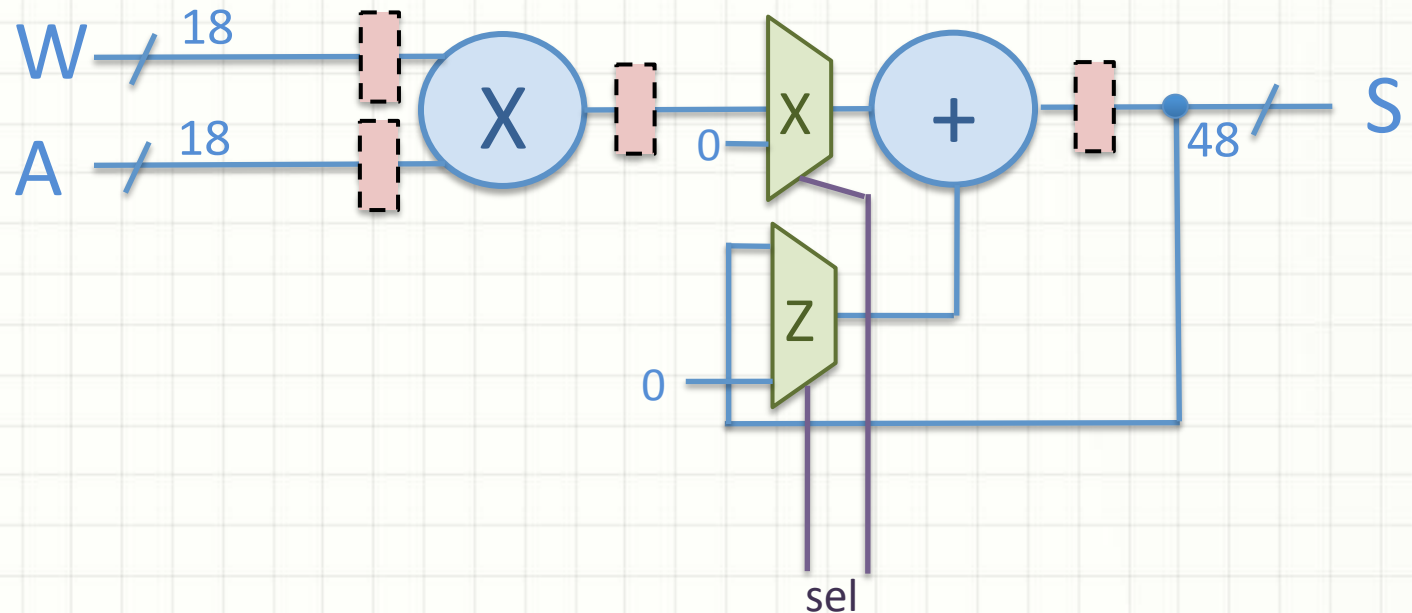


Timings with registers

 

Timings with pipelining

 


Weighted sum, sliding window

 

non-pipelined

Weighted sum, sliding window

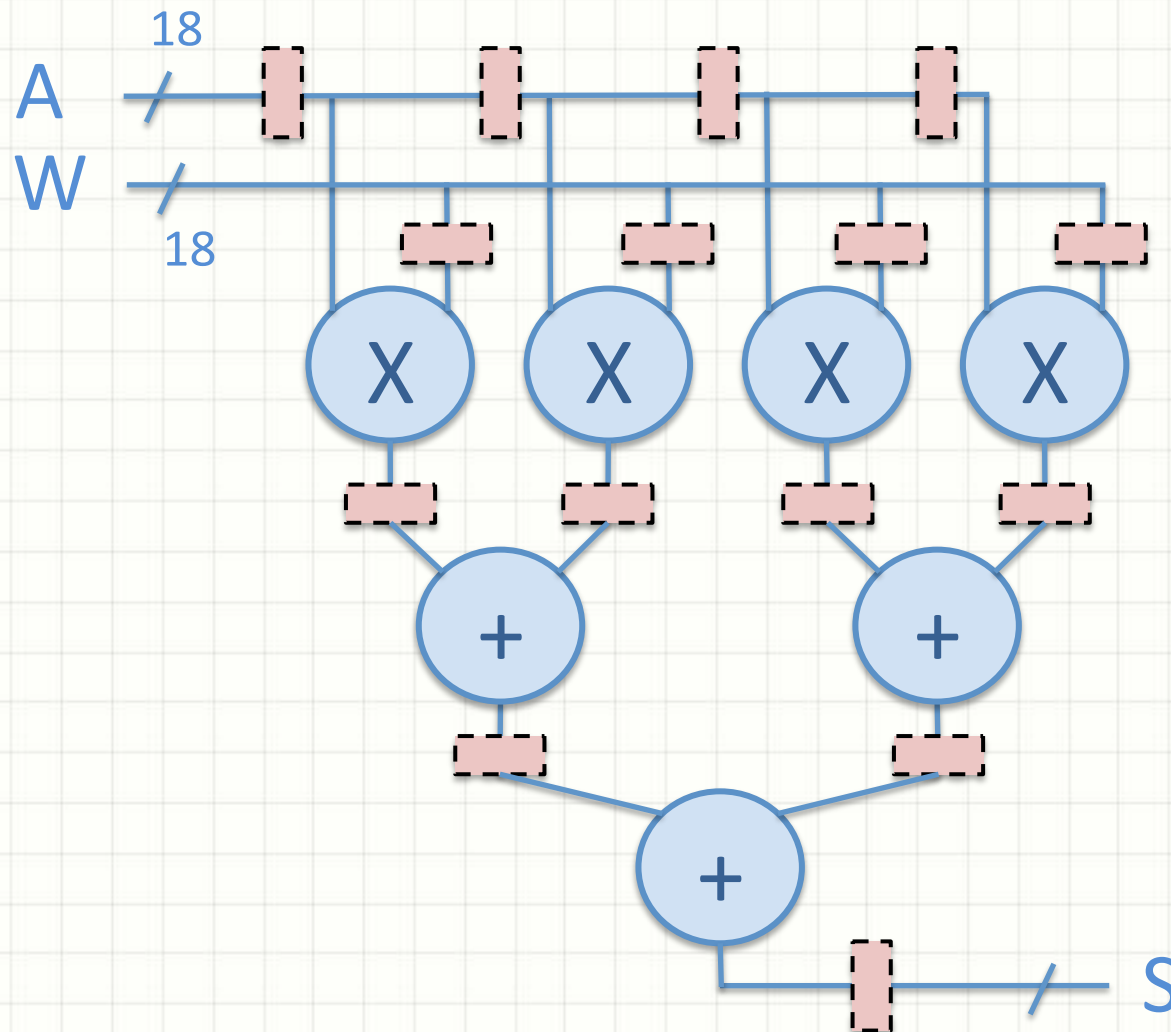



THANKS